

# Today's topic:

1. Basic current mirrors
2. single-stage amplifiers
3. differential amplifiers

Chapter 3

The purpose of this Chapter is to discuss fundamental circuit building blocks.

A good knowledge of these basic building blocks is critical to understanding many subjects to be discussed later.

CMOS current mirrors and gain stages are emphasized here, while the general small-signal analysis method can be applied to BJT versions.

When analyzing transistor circuits to determine their small-signal behavior, it is implicitly assumed that signals are small enough that linear approximations about an operating point (Q point) accurately reflect how the circuit operates. These linear approximations may be represented schematically by replacing transistors with small-signal equivalent circuit, whose parameters (such as  $g_m$ ,  $r_{ds}$  etc) are determined from the operating point.

A note on notations in the book and the lecture:

To the extent possible in this chapter, operating point quantities are represented with uppercase voltage and current symbols (e.g.,  $V_{GS}$ ,  $I_D$ ) and small-signal quantities with lowercase symbols (e.g.,  $v_{gs}$ ,  $i_d$ ). However, the practicing designer must always be alert to imprecise notation and remain able to interpret meanings within their proper context.

## A general procedure for small-signal analysis:

- a.** Set all signal sources to zero and perform an operating point analysis for all currents and voltages. A voltage source set to 0 V is the same as an ideal wire—a short circuit. A current source set to 0 A is the same as an open circuit.
- b.** Replace all transistors with their small-signal equivalents where the parameters  $g_m$ ,  $r_{ds}$ , etc, are found from the operating point voltages and currents using the relationships in summarized in Section 1.3.
- c.** Set all independent sources equal to zero, except for the signal sources that were zeroed in step (a). This includes power supply voltages, bias currents, etc. Remember that setting a voltage source to zero means replacing it with a short circuit, and setting a current source to zero means replacing it with an open circuit.
- d.** Analyze the resulting linearized small-signal circuit to find small-signal node voltages, branch currents, small-signal resistances, etc.
- e.** If desired, the complete solution may be found by superimposing the results of the operating point analysis in step (a) and those of small-signal analysis in step (d). The result so obtained is approximate because the small-signal analysis approximates transistor nonlinear behavior with linearized models.

## A general procedure for small-signal analysis:

- a.** Set all signal sources to zero and perform an operating point analysis for all currents and voltages. A voltage source set to 0 V is the same as an ideal wire—a short circuit. A current source set to 0 A is the same as an open circuit.
- b.** Replace all transistors with their small-signal equivalents where the parameters  $g_m$ ,  $r_{ds}$ , etc, are found from the operating point voltages and currents using the relationships in summarized in Section 1.3.
- c.** Set all independent sources equal to zero, except for the signal sources that were zeroed in step (a). This includes power supply voltages, bias currents, etc. Remember that setting a voltage source to zero means replacing it with a short circuit, and setting a current source to zero means replacing it with an open circuit.
- d.** Analyze the resulting linearized small-signal circuit to find small-signal node voltages, branch currents, small-signal resistances, etc.
- e.** If desired, the complete solution may be found by superimposing the results of the operating point analysis in step (a) and those of small-signal analysis in step (d). The result so obtained is approximate because the small-signal analysis approximates transistor nonlinear behavior with linearized models.

# 3.1 A simple current mirror


An ideal current mirror is a two port circuit that accepts an input current  $I_{in}$  and produce an output current  $I_{out}=I_{in}$ .

Also, an ideal current mirror will have zero input resistance but high output resistance.

Both transistors are in active region (so the drain voltage of Q2 must be larger than  $V_{eff2}$ ).

If Q1 and Q2 have the same size, and finite  $r_{ds}$  is ignored, then Q1 and Q2 have the same current (due to the same  $V_{gs}$ )

 However, when  $r_{ds}$  are considered, the transistor with larger  $V_{ds}$  will have larger current.



Chapter 3 Figure 01

# A simple current mirror: input resistance


We can use the following small-signal equivalent circuit to compute the input resistance of the current mirror. ( $I_{in}$  is open and low-frequency model is used).

Then, apply a test signal voltage  $V_y$  at node  $V_1$  and measure the current  $i_y$

$$i_y = \frac{V_y}{r_{ds1}} + g_{m1}v_{gs1} = \frac{V_y}{r_{ds1}} + g_{m1}V_y$$

Input resistance is given by  $r_{in} = V_y/i_y = 1/g_{m1} \parallel r_{ds1} \cong 1/g_{m1}$

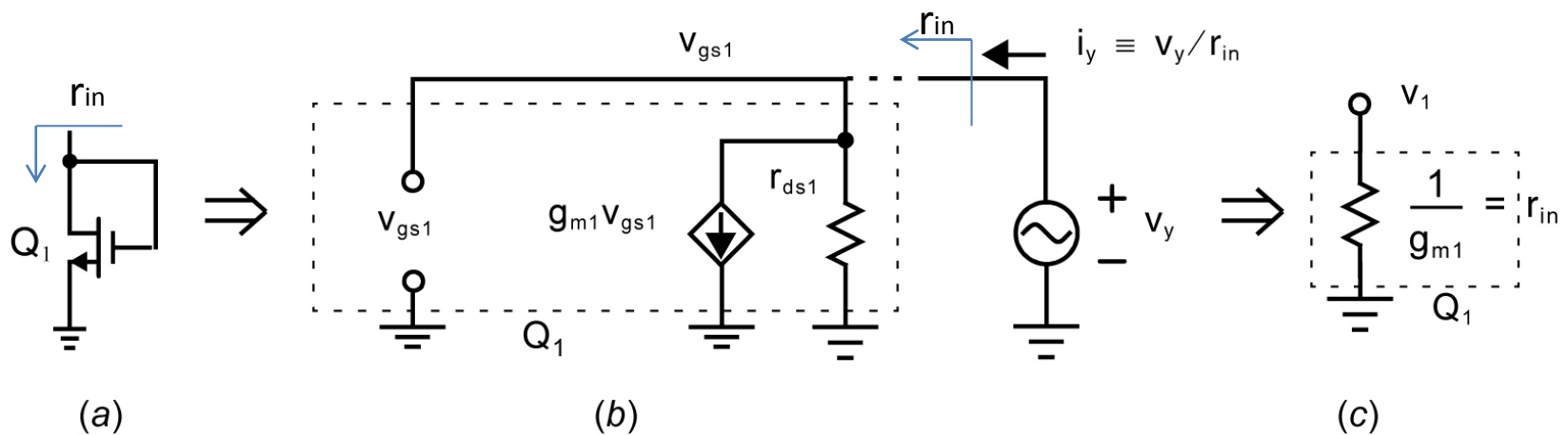$Q_1$  is sometimes referred to as a diode-connected transistor.




Chapter 3 Figure 02
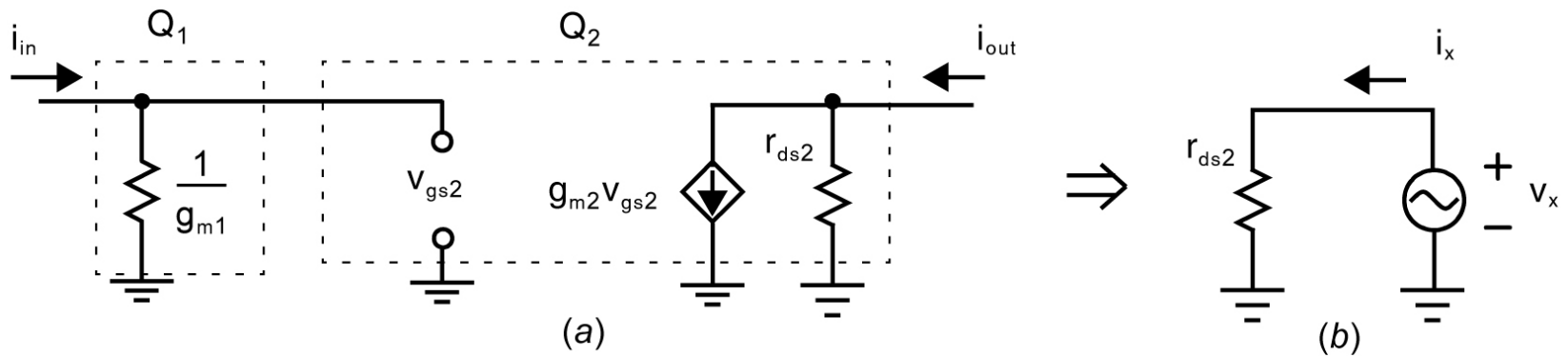
# A simple current mirror: output resistance

Using the model for the input resistance from previous slides leads to a simplified small-signal equivalent circuit for the overall current mirror. .

Output resistance is given by  $r_{out} = V_x / i_x = r_{ds2}$



Chapter 3 Figure 03

 


Figure 01


$$r_{out} = r_{ds2}$$

In this configuration, as long as gate terminal is small-signal ground, the resistance looking into the drain is  $r_{ds2}$
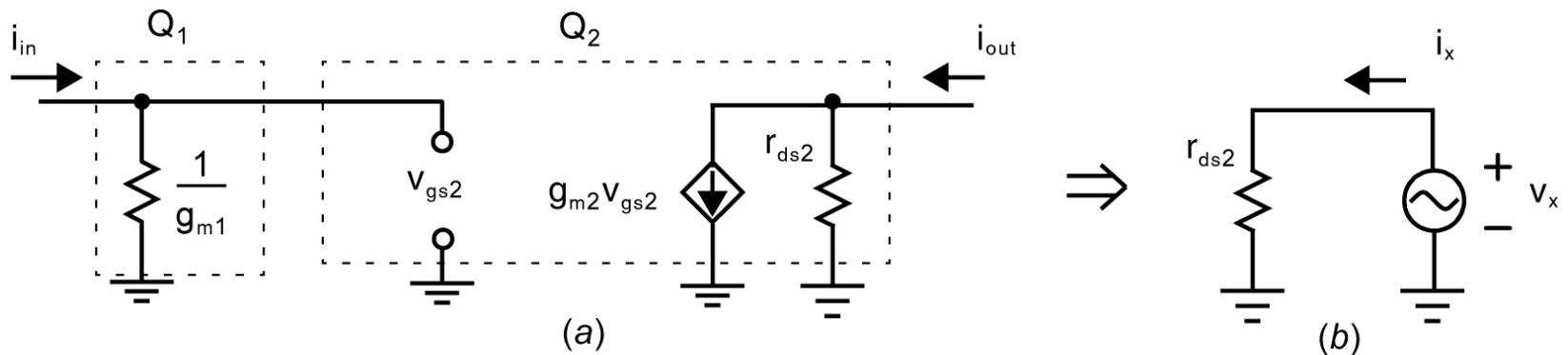
# A simple current mirror: output resistance

Using the model for the input resistance from previous slides leads to a simplified small-signal equivalent circuit for the overall current mirror. .

Output resistance is given by  $r_{out} = V_x / i_x = r_{ds2}$



Chapter 3 Figure 03



## An example 3.1 (page 119)

Consider the current mirror shown in Fig. 3.1, where  $I_{in} = 100 \mu\text{A}$  and each transistor has  $W/L = 10 \mu\text{m}/0.4 \mu\text{m}$ . Given the 0.35- $\mu\text{m}$  CMOS device parameters in Table 1.5, find  $r_{out}$  for the current mirror and the value of  $g_{m1}$ . Also, estimate the change in  $I_{out}$  for a 100 mV change in the output voltage. What voltage must be maintained at the drain of  $Q_2$  to ensure it remains in active mode?

$$r_{out} = r_{ds2} = \frac{L}{\lambda L I_D} = \frac{0.4 \mu\text{m}}{(0.16 \mu\text{m/V})(100 \mu\text{A})} = 25 \text{ k}\Omega$$

$$g_{m1} = \sqrt{2\mu_n C_{ox}(W/L)I_{D1}} = 0.97 \text{ mA/V}$$

$$r_{s1} = 1/g_{m1} \cong 1.03 \text{ k}\Omega.$$

$$\Delta I_{out} = \frac{\Delta V}{r_{out}} = \frac{100 \text{ mV}}{25 \text{ k}\Omega} = 4 \mu\text{A}$$

← Estimation using low-frequency small-signal linear equivalent circuit


$$V_{eff2} = \sqrt{\frac{2I_D}{\mu_n C_{ox}(W/L)}} = 205 \text{ mV}$$

## 3.2 A common-source amplifier

A common use of simple current mirrors is to be active loads in a single-stage amplifier.

By using an active load, a high-impedance output load can be realized without using excessively large resistors or a large power supply voltage (for example, a 100k resistor load with 100 $\mu$ A bias current would need a power supply of at least 10V).

 The common-source (CS) topology is the most popular gain stage, especially when high input impedance is desired.



Chapter 3 Figure 04

# Small-signal analysis of CS: DC gain $A_v$

Assume that all transistors are in active region, the small-signal model of the CS amplifier with active load is shown below:


(note the resistance  $R_2$  is made up of parallel of  $r_{ds1}$  and  $r_{ds2}$ .)

$$A_V = \frac{V_{out}}{V_{in}} = -g_{m1} R_2 = -g_{m1} (r_{ds1} \parallel r_{ds2})$$


Depending on device sizes, currents and technology used, the typical gain for a CS amplifier could be between -5 to -100.

$A_v$  is about one half of the intrinsic gain of Q1:  $A_i = g_{m1} r_{ds1} \approx 2/(\lambda V_{eff})$ . if  $r_{ds2} \approx r_{ds1}$

 
To maximize the gain, it is desirable to minimize  $V_{eff1}$ . For a fixed bias current, this is to increase  $W$ ?


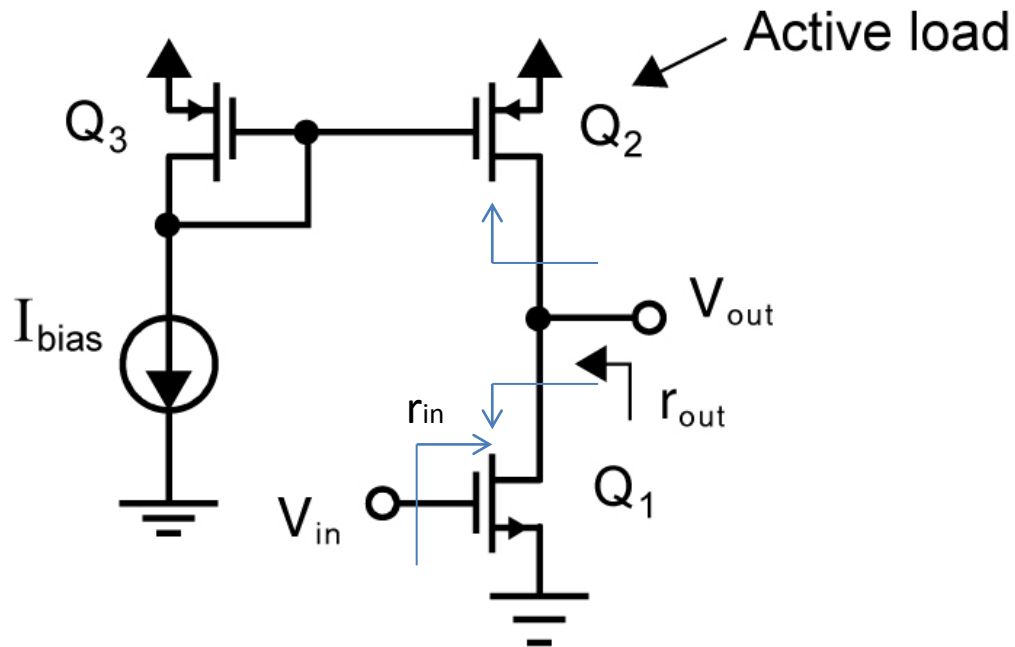
# Small-signal analysis of CS: $r_{in}$ and $r_{out}$



Chapter 3 Figure 04

 

Chapter 3 Figure 05

## An example 3.2 and 3.3 (page 121)

Assume  $I_{\text{bias}} = 100 \mu\text{A}$ , all transistors have  $W/L = 10 \mu\text{m}/0.4 \mu\text{m}$  in Fig. 3.4, and the device parameters are those of the 0.35- $\mu\text{m}$  CMOS process in Table 1.5. What is the gain of the stage?

$$g_{m1} = \sqrt{2\mu_n C_{\text{ox}}(W/L)_1 I_{\text{bias}}} = 0.97 \text{ mA/V}$$

$$r_{ds1} = r_{ds2} = \frac{L}{\lambda L I_D} = \frac{0.4 \mu\text{m}}{(0.16 \mu\text{m/V})(100 \mu\text{A})} = 25 \text{ k}\Omega$$

$$A_V = -g_{m1}(r_{ds1} \parallel r_{ds2}) = -0.97 \text{ mA/V}(25 \text{ k}\Omega \parallel 25 \text{ k}\Omega) = -12.1 \text{ V/V}$$

Modify the design in Example 3.2 to increase the gain by 20% by changing only the device width,  $W$ .

Neglecting higher-order effects, with the drain current fixed the output resistance ( $r_{ds1} \parallel r_{ds2}$ ) is nominally unchanged. Hence, in order to increase gain by 20%, we must increase  $g_{m1}$  by 20%. Due to the square-root dependence of  $g_m$  on  $W$  (with fixed current), this in turn requires a 44% increase in  $W_1$ . Hence, the new size of  $Q_1$  is (14.4  $\mu\text{m}/0.4 \mu\text{m}$ ). The resulting gain is


$$g_{m1} = \sqrt{2\mu_n C_{\text{ox}}(W/L)_1 I_{\text{bias}}} = 1.17 \text{ mA/V}$$
$$\Rightarrow A_V = -g_{m1}(r_{ds1} \parallel r_{ds2}) = -1.17 \text{ mA/V}(25 \text{ k}\Omega \parallel 25 \text{ k}\Omega) = -14.6 \text{ V/V}$$

$$V_{\text{eff1}} = \sqrt{\frac{2I_D}{\mu_n C_{\text{ox}}(W/L)}} = 171 \text{ mV}$$
 
## 3.3 A common-drain amplifier

Another general use of current mirrors is to supply the bias current for a common-drain or source follower (SF) amplifier.

SF amplifiers are commonly used as voltage buffers.



Chapter 3 Figure 06


# Small-signal analysis of SF amplifier: gain $A_v$

In the small-signal model, note that the voltage-controlled current source that models the body effect of MOS transistors is included as there is finite source-body voltage (unlike CS amplifier), which may become a major limitation on the small-signal gain.

Note that the voltage-controlled current source modeling the body effect produces a current that is proportional to the voltage across it, which makes it equivalent to a resistor of  $1/g_{s1}$ . This allows to simplify the circuit to the right-hand side.

$$v_{out}/R_{s1} - g_{m1}(v_{in} - v_{out}) = 0$$


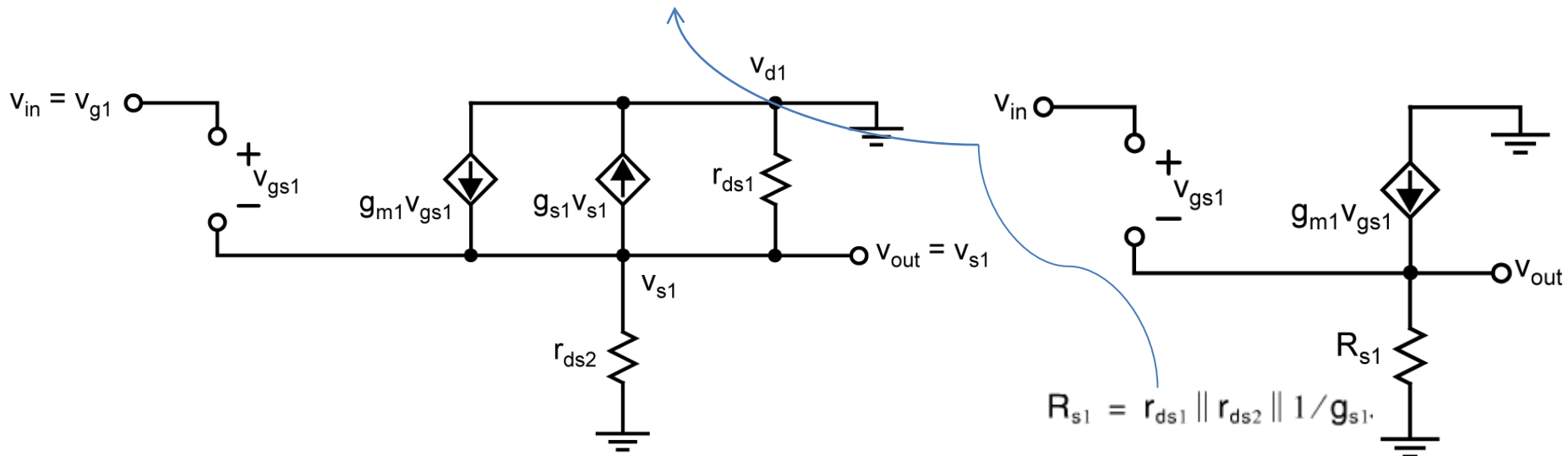
$$A_v = \frac{v_{out}}{v_{in}} = \frac{g_{m1}}{g_{m1} + G_{s1}} = \frac{g_{m1}}{g_{m1} + g_{s1} + g_{ds1} + g_{ds2}} = g_{m1} \left( \frac{1}{g_{m1}} \parallel \frac{1}{g_{s1}} \parallel r_{ds1} \parallel r_{ds2} \right)$$



Chapter 3 Figure 07

Chapter 3 Figure 08
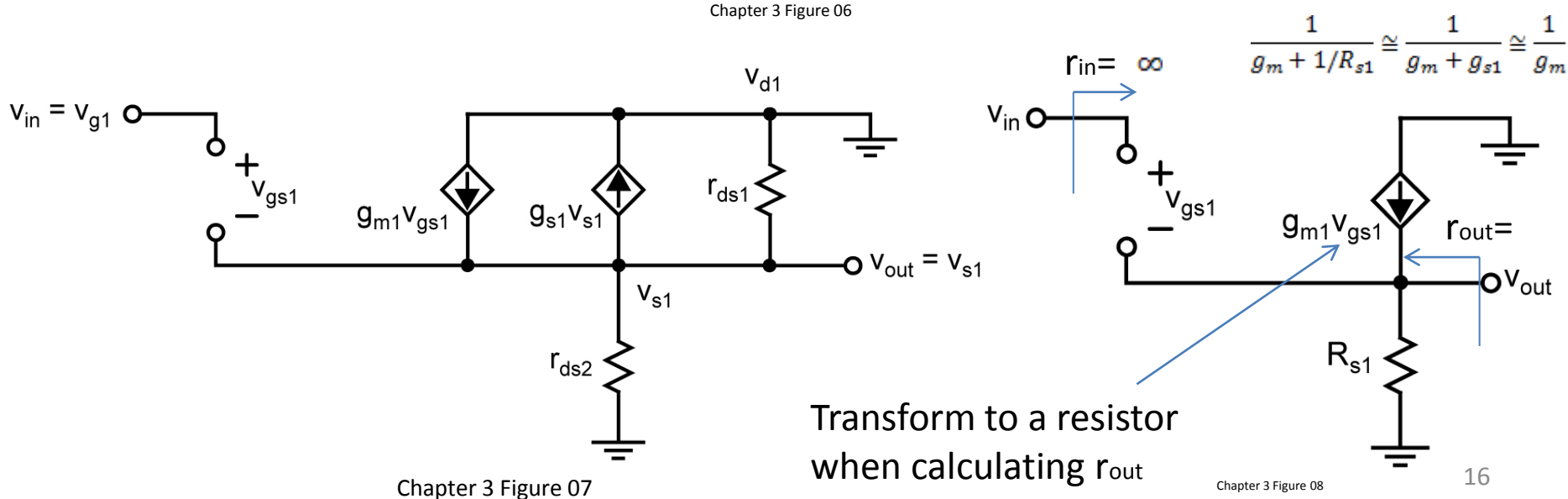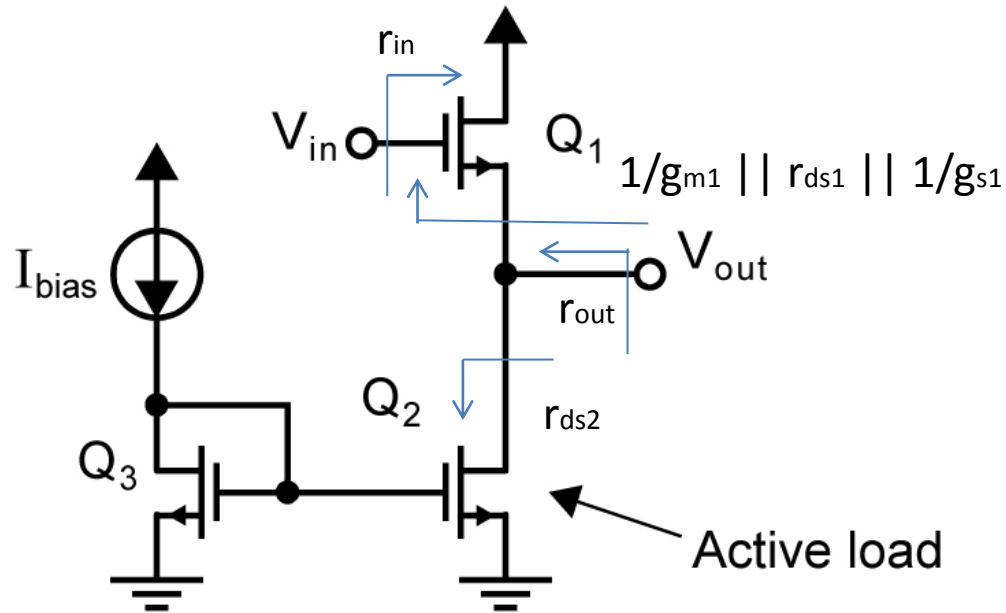
# Small-signal analysis of SF: $r_{in}$ and $r_{out}$





# Example 3.4 (page 123)

Consider the source follower of Fig. 3.6 where  $I_{bias} = 100 \mu A$ , all transistors have  $W/L = 2 \mu m/0.2 \mu m$ ,  $\phi_F \cong 0.4 V$  and  $\gamma = 0.3 V^{-1/2}$ , and the other device parameters are those of the 0.18- $\mu m$  CMOS process in Table 1.5. What is the gain of the stage? assume that  $V_{SB} \approx 0.5 V$

$$g_{m1} = \sqrt{2\mu_n C_{ox}(W/L)_1 I_{bias}} = 0.735 \text{ mA/V}$$

$$r_{ds1} = r_{ds2} = \frac{L}{\lambda L I_D} = \frac{0.2 \mu m}{(0.08 \mu m/V)(100 \mu A)} = 25 \text{ k}\Omega$$

$$g_{s1} = \frac{\gamma g_m}{2\sqrt{V_{SB} + |2\phi_F|}}$$

$$g_{s1} = \frac{0.3 V^{-1/2} \cdot g_m}{2\sqrt{0.5 V + 0.8 V}} \cong 0.13 g_m = 0.1 \text{ mA/V}$$

$$A_V = \frac{0.735 \text{ mA/V}}{0.735 \text{ mA/V} + 0.1 \text{ mA/V} + 0.04 \text{ mA/V} + 0.04 \text{ mA/V}} = 0.8 \text{ V/V} = -1.9 \text{ dB}$$


0.18 $\mu m$	
NMOS	PMOS
270	70
0.45	-0.45
0.08	0.08
8.5	8.5
5	5
1.6	1.7
1.7	1.0
1.6	2.4
0.35	0.35
0.50	0.55

Hence, it can be seen that body-effect is the major source of error causing the gain of the SF amplifier to be less than 1.0.

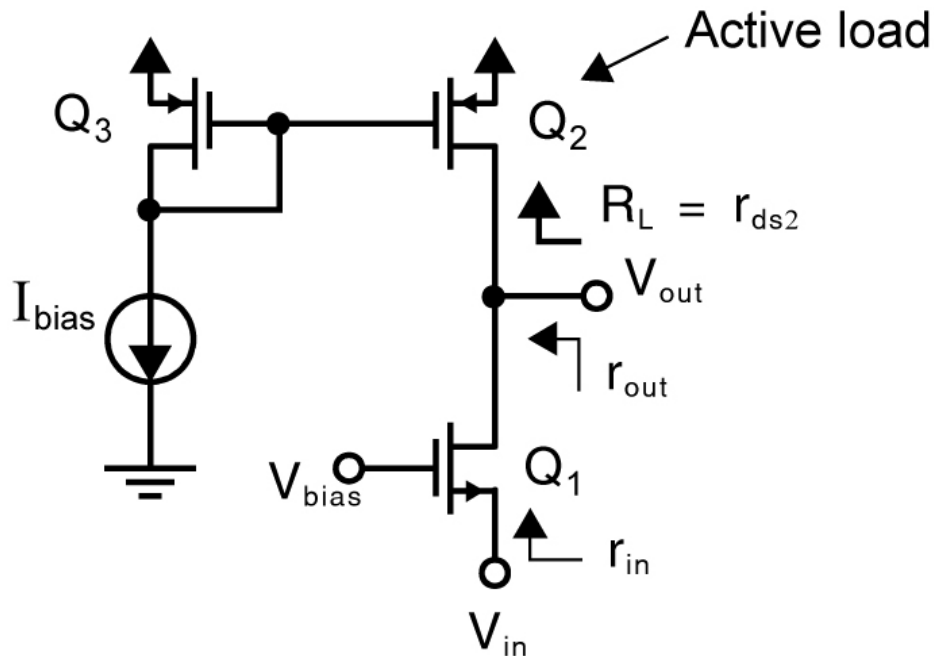
## 3.4 A common-gate amplifier

A common-gate amplifier is used as a gain stage when small input impedance is desired. Also, it is often used when the input signal is a current as small input impedance is desired.


Aside from its low input impedance, the common-gate amplifier is similar to a CS amplifier as the input signal is across Gate-Source terminal and output taken from the Drain terminal. Hence, in both amplifiers, the small signal gain equals the product of  $g_m$  and total impedance at the drain.




Chapter 3 Figure 09

 

Chapter 3 Figure 10

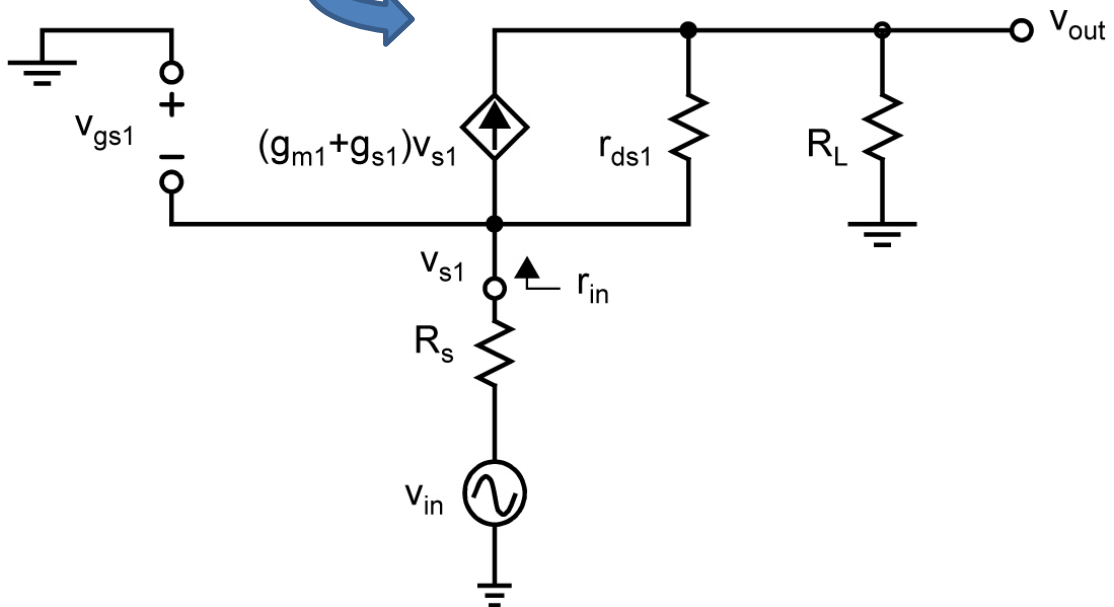

Chapter 3 Figure 11

 

Chapter 3 Figure 11

$$v_{out}(G_L + g_{ds1}) - v_{s1}g_{ds1} - (g_{m1} + g_{s1})v_{s1} = 0$$


$$\longrightarrow \frac{v_{out}}{v_{s1}} = \frac{g_{m1} + g_{s1} + g_{ds1}}{G_L + g_{ds1}} = (g_{m1} + g_{s1} + g_{ds1})(R_L \parallel r_{ds1}) \cong g_{m1}(R_L \parallel r_{ds1})$$

$$i_s = v_{s1}(g_{m1} + g_{s1} + g_{ds1}) - v_{out}g_{ds1}$$


$$\longrightarrow g_{in} \equiv \frac{i_s}{v_{s1}} \equiv \frac{g_{m1} + g_{s1} + g_{ds1}}{1 + \frac{g_{ds1}}{G_L}}$$

$$r_{in} = \frac{1}{g_{in}} = \left( \frac{1}{g_{m1}} \parallel \frac{1}{g_{s1}} \parallel r_{ds1} \right) \left( 1 + \frac{R_L}{r_{ds1}} \right) \cong \frac{1}{g_{m1}} \left( 1 + \frac{R_L}{r_{ds1}} \right)$$

# Comparison of the impedances

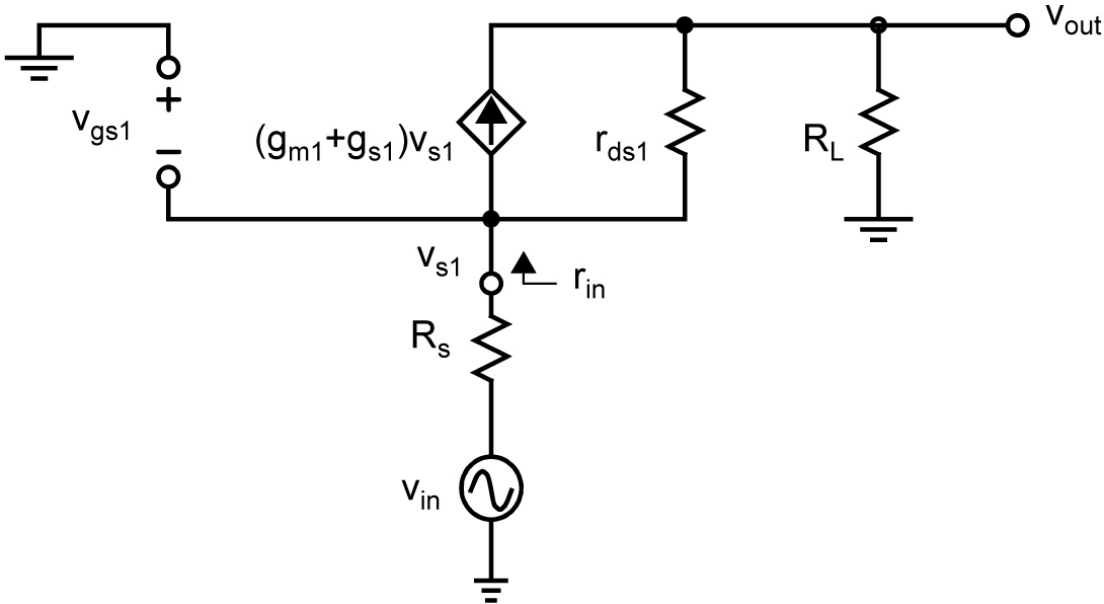

Chapter 3 Figure 11

 


Chapter 3 Figure 08

$$\longrightarrow \quad g_{in} \equiv \frac{i_s}{v_{s1}} \equiv \frac{g_{m1} + g_{s1} + g_{ds1}}{1 + \frac{g_{ds1}}{G_L}}$$

$$r_{in} = \frac{1}{g_{in}} = \left( \frac{1}{g_{m1}} \parallel \frac{1}{g_{s1}} \parallel r_{ds1} \right) \left( 1 + \frac{R_L}{r_{ds1}} \right) \cong \frac{1}{g_{m1}} \left( 1 + \frac{R_L}{r_{ds1}} \right) \longleftarrow \text{Compare to Slide 16}$$

If  $R_L = r_{ds2} = r_{ds1}$ ,  $r_{in} = 2/g_{m1}$  for low frequency. If  $R_L$  is even larger, then  $r_{in}$  is more than  $2/g_{m1}$ . 21

# Small-signal analysis of CG: $r_{out}$

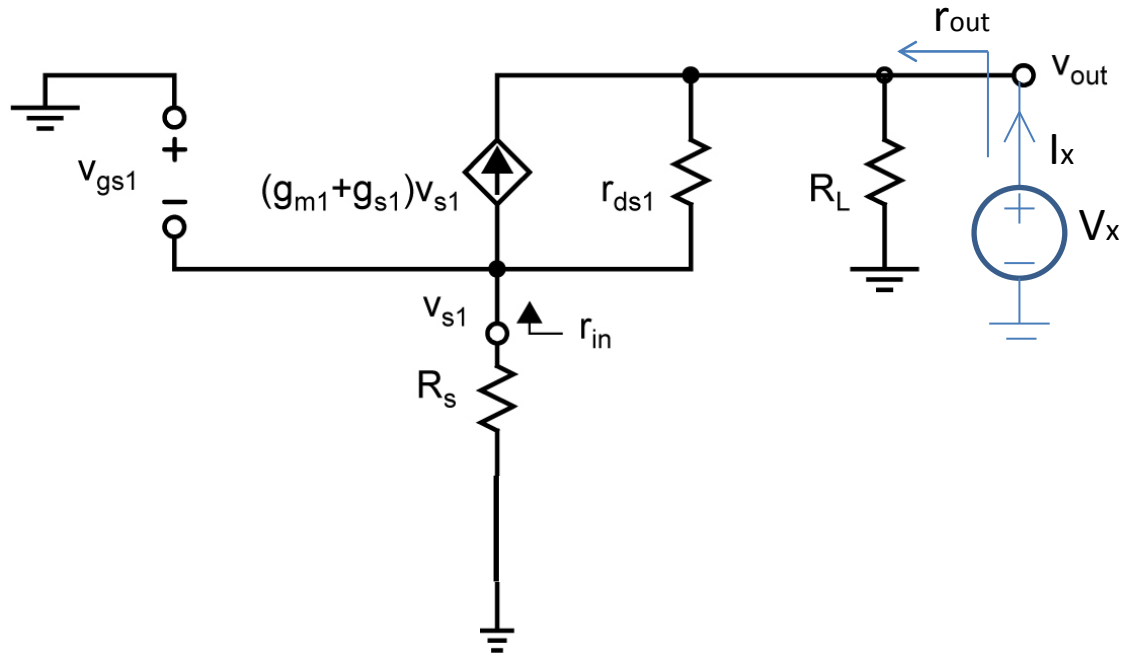

Chapter 3 Figure 11

$$\left\{ \begin{array}{l} I_x = V_x/R_L - (g_{m1} + g_{s1})V_{s1} + (V_x - V_{s1})/r_{ds1} \\ -(g_{m1} + g_{s1})V_{s1} + (V_x - V_{s1})/r_{ds1} = V_{s1}/R_s \end{array} \right. \longrightarrow r_{out} = \frac{V_x}{I_x} = \frac{[1 + (g_m + g_{s1})R_s + \frac{R_s}{r_{ds1}}]r_{ds1}R_L}{R_L + r_{ds1}}$$

If  $R_L = r_{ds2} = r_{ds1}$  and  $R_s = 0$ , then not surprisingly  $r_{out} = r_{ds1}/2$

# Example 3.5 (page 127)

Design the common-gate amplifier of Fig. 3.9 to have an input impedance of approximately  $50 \Omega$  using the  $0.18\text{-}\mu\text{m}$  CMOS devices in Table 1.5 with  $I_{\text{bias}} = 100 \mu\text{A}$ ,  $(W/L)_3 = 2 \mu\text{m}/0.2 \mu\text{m}$ .

Since  $(\lambda L)_1 = (\lambda L)_2$ , if we take  $L_1 = L_2 = 0.2 \mu\text{m}$  we ensure  $r_{\text{ds}2} = R_L = r_{\text{ds}1}$

$$r_{\text{in}} \cong 2/g_{\text{m}1}$$

Hence, to ensure  $r_{\text{in}} = 50 \Omega$ ,

$$g_{\text{m}1} \cong 2/(50 \Omega) = 40 \text{ mA/V}$$

If we take  $V_{\text{eff}1} = 200 \text{ mV}$ ,

$$I_{\text{D}2} = I_{\text{D}1} = g_{\text{m}1} V_{\text{eff}1}/2 = (40 \text{ mA/V})(200 \text{ mV})/2 = 4 \text{ mA}$$

This requires the current mirror to provide a gain of  $4 \text{ mA}/100 \mu\text{A} = 40$ .

$$(W/L)_2 = 40(W/L)_3 = 80 \mu\text{m}/0.2 \mu\text{m}$$


$$(W/L)_1 = \frac{g_{\text{m}1}^2}{2\mu_n C_{\text{ox}} I_{\text{D}1}} = 148 \mu\text{m}/0.2 \mu\text{m}$$

<b>0.18 <math>\mu\text{m}</math></b>	
<b>NMOS</b>	<b>PMOS</b>
270	70
0.45	-0.45
0.08	0.08
8.5	8.5
5	5
1.6	1.7
1.7	1.0
1.6	2.4
0.35	0.35
0.50	0.55

 
# 3.5 Source-degenerated current mirrors

Simple current mirrors presented before have relatively small output impedance.


To increase this output impedance, a source degenerated current mirror can be used.



Chapter 3 Figure 12

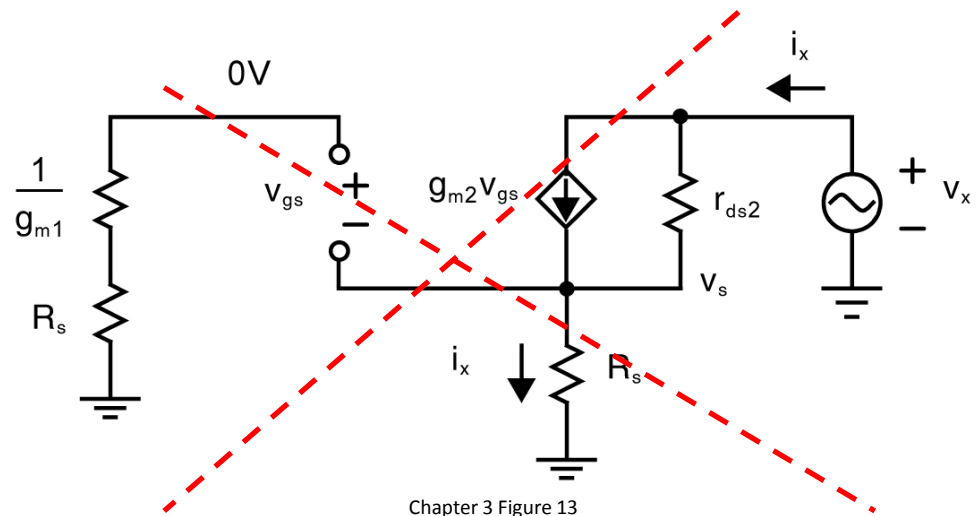

Chapter 3 Figure 13

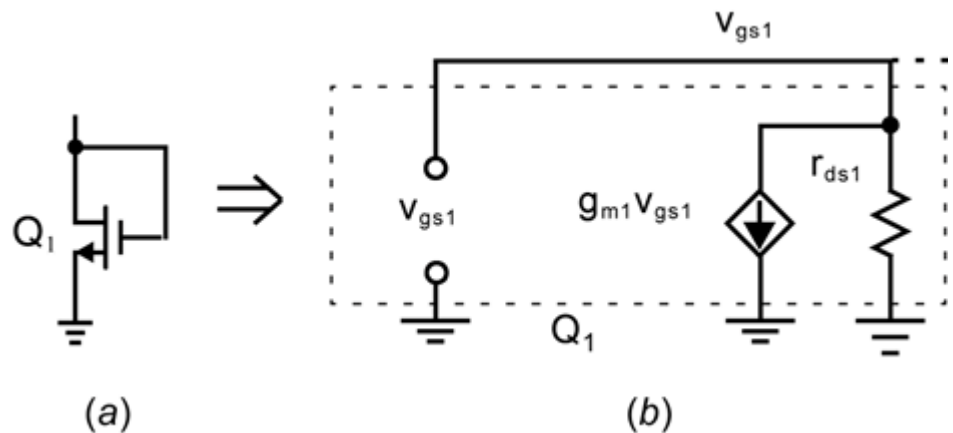



# Small-signal model to find $r_{out}$

Note that in the small-signal model to compute  $r_{out}$ , (1) the gate voltage for both Q1 and Q2 is 0 as no small-signal current flows to the gate, (2) we neglect the body effect.


$$v_s = i_x R_s$$

$$v_{gs} = -v_s \quad \leftarrow \quad g_{m1} V_{gs1} = V_{gs1}/r_{ds1}$$

$$i_x = g_{m2} v_{gs} + \frac{v_x - v_s}{r_{ds2}} \quad i_x = -i_x g_{m2} R_s + \frac{v_x - i_x R_s}{r_{ds2}}$$

$$r_{out} = \frac{v_x}{i_x} = r_{ds2} [1 + R_s (g_{m2} + g_{ds2})] \cong r_{ds2} (1 + R_s g_{m2}) \cong r_{ds2} [1 + R_s (g_{m2} + g_{s2})] \quad \text{If body effect included}$$

Compare to Slides 22

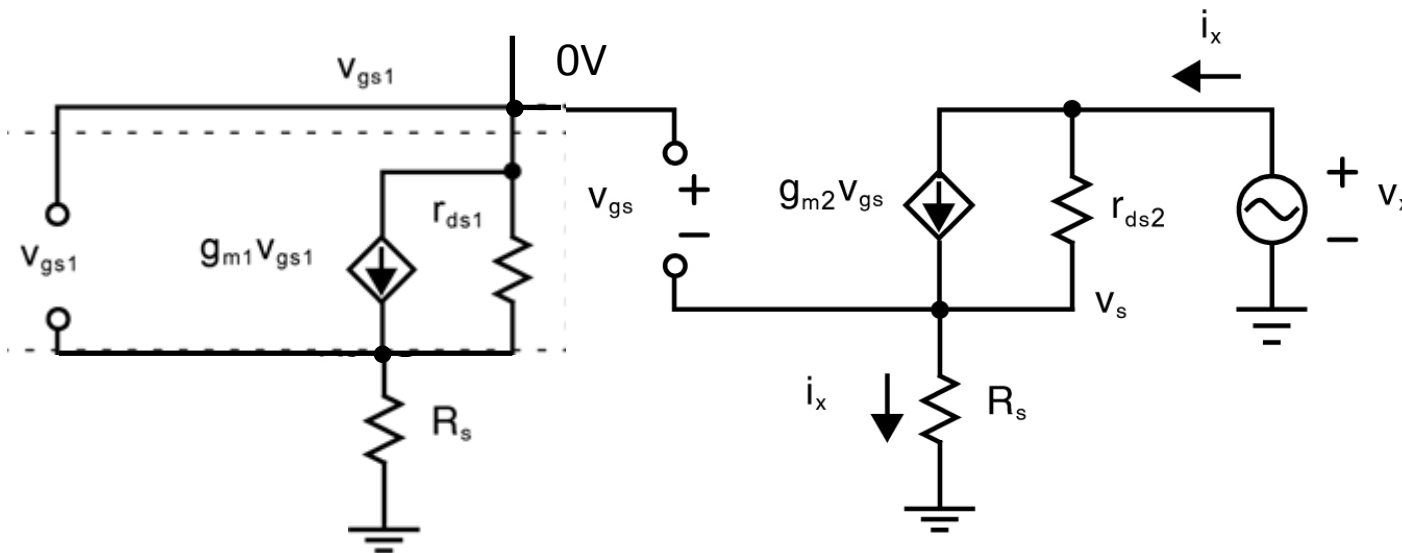

Chapter 3 Figure 13

## Example 3.6 (page 128)

Consider the current mirror shown in Fig. 3.12, where  $I_{in} = 100 \mu\text{A}$ , each transistor has  $W/L = 10 \mu\text{m}/0.2 \mu\text{m}$ , and  $R_s = 1 \text{ k}\Omega$ . Using the 0.18- $\mu\text{m}$  CMOS devices in Table 1.5, find  $r_{out}$  for the current mirror. Assume the body effect can be approximated by  $g_s = 0.15g_m$ .

Nominally,  $I_{out} = I_{in}$ , and thus we find the small-signal parameters for this current mirror to be

$$g_{m2} = \sqrt{2\mu_n C_{ox}(W/L)I_{out}} = 1.64 \text{ mA/V}$$

Also we have

$$r_{ds2} = \frac{0.2 \mu\text{m}}{0.08 \mu\text{m/V} \cdot 100 \mu\text{A}} = 25 \text{ k}\Omega$$

$$r_{out} = 25 \text{ k}\Omega \left[ 1 + 1 \text{ k}\Omega \left( 1.64 \text{ mA/V} + 0.15 \cdot 1.64 \text{ mA/V} + \frac{1}{25 \text{ k}\Omega} \right) \right] = 73.15 \text{ k}\Omega$$

Also note that the voltage drop across  $R_s$  equals  $100 \mu\text{A} \times 1 \text{ k}\Omega = 0.1 \text{ V}$

Therefore, compared to the simple two-transistor current mirror, the output impedance of source-degenerated current mirror has output impedance increased by a factor equal to  $(1+g_{m2}R_s)$ .


Note also that such a formula can often be applied to moderately complicated circuits to quickly estimate the impedance looking into a node.

# 3.6 Cascode current mirrors

Cascode current mirrors can be used to further increase the output impedance.

Note that  $r_{out}'$  looking into the drain of Q2 is simply  $r_{ds2}$ .

 The  $r_{out}$  looking into the drain of Q4, can be derived from the formula for source-degenerated current mirrors, by considering Q4 as a current source with a source-degenerated resistor of  $r_{ds2}$  from Q2.



$$r_{out} = r_{ds4}[1 + R_s(g_{m4} + g_{s4} + g_{ds4})]$$

where now  $R_s = r_{ds2}$ . Therefore, the output impedance is given by


$$r_{out} = r_{ds4}[1 + r_{ds2}(g_{m4} + g_{s4} + g_{ds4})]$$

$$\cong r_{ds4}[1 + r_{ds2}(g_{m4} + g_{s4})]$$

$$\cong r_{ds4}(r_{ds2}g_{m4})$$

Thus, the output impedance is increased by a factor of  $g_{m4}r_{ds4}$ , which is the gain of a single transistor. Such a large increase can be important to realize single-stage amplifiers with large gains.

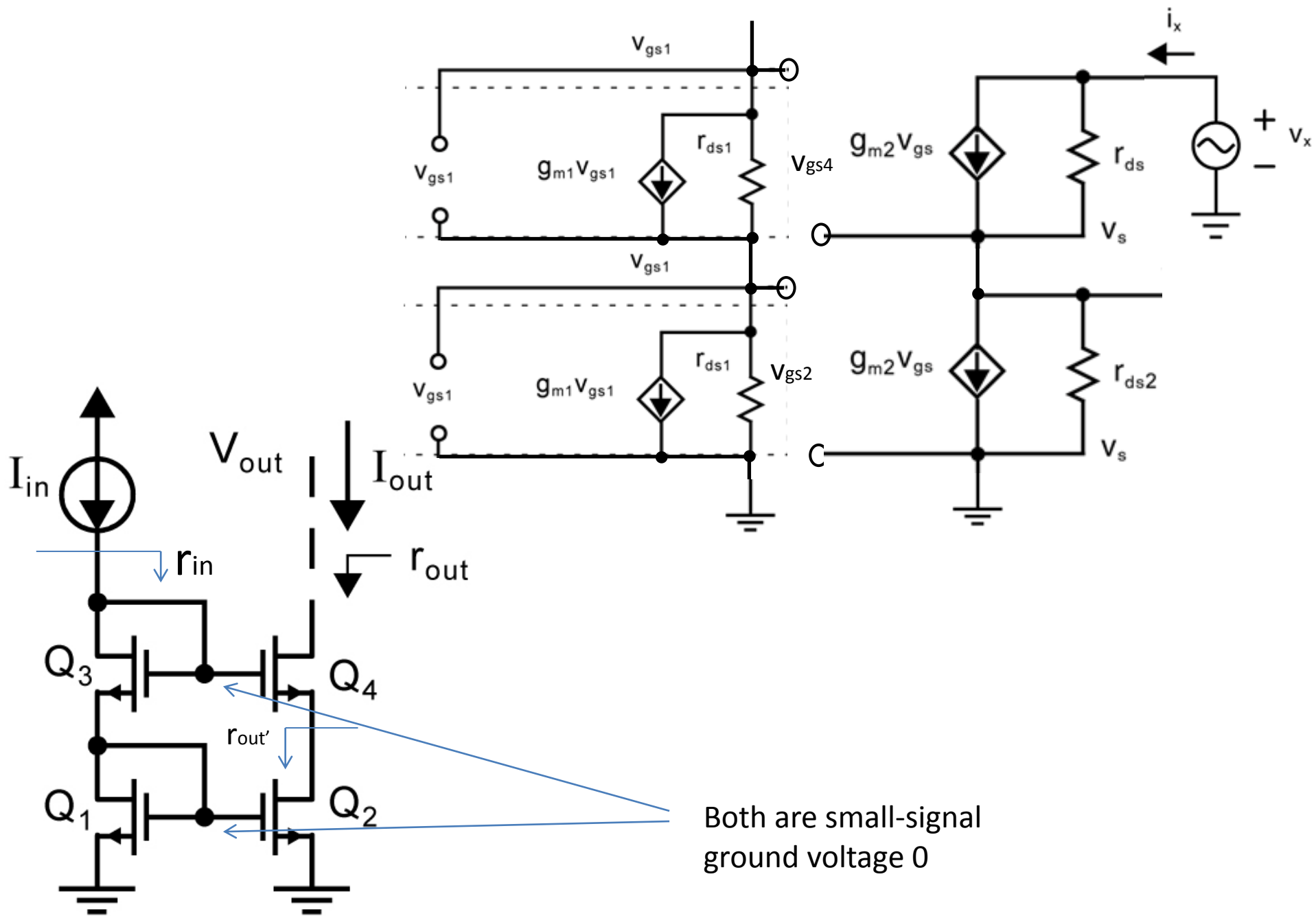The drawback in using a cascode current mirror is the reduction of the maximum output voltage swing.




Chapter 3 Figure 14

# Minimum output voltage

What is the minimum voltage at  $V_{out}$  to maintain Q2 and Q4 in active region? If we assume all transistors have the same sizes and currents, and therefore the same  $V_{gsi}=V_{effi}+V_{tni}$ , where  $i=1,2,3,4$ , then

$$V_{G3} = V_{GS1} + V_{GS3} = 2V_{eff} + 2V_{tn}$$
 
$$V_{DS2} = V_{G3} - V_{GS4} = V_{G3} - (V_{eff} + V_{tn}) = V_{eff} + V_{tn}$$



So, the  $V_{ds2}$  for Q2 is larger than the minimum needed which is  $V_{eff2}$ .

Since the smallest output voltage  $V_{D4}$  can be  $V_{DS2}+V_{eff2}$  before Q4 goes into triode region, so the minimum allowed voltage for  $V_{out}$  is

$$V_{out} > V_{DS2} + V_{eff} = 2V_{eff1} + V_{tn}$$

The loss of signal swing is a serious drawback when modern analog IC are used with low power supply of 1V. (Later, we will see how to address this issue).

# Example 3.7 (page 130)

Consider the cascode current mirror shown in Fig. 3.14, where  $I_{in} = 100 \mu A$  and each transistor has  $W/L = 10 \mu m / 0.4 \mu m$ . Given the 0.35- $\mu m$  CMOS device parameters in Table 1.5, find  $r_{out}$  for the current mirror (approximating the body effect by  $0.2g_m$ ). Also find the minimum output voltage at  $V_{out}$  such that the output transistors remain in the active region.

Nominally,  $I_{out} = I_{in}$ , and thus we can find the small-signal parameters for this current mirror to be


$$g_{m4} = \sqrt{2\mu_n C_{ox}(W/L)I_{out}} = 0.97 \text{ mA/V}$$

$$r_{ds2} = r_{ds4} = \frac{0.4 \mu m}{0.16 \mu m/V \cdot 100 \mu A} = 25 \text{ k}\Omega$$

$$r_{out} = 25 \text{ k}\Omega [25 \text{ k}\Omega (0.97 \text{ mA/V} + 0.2 \times 0.97 \text{ mA/V} + 1/25 \text{ k}\Omega)] = 753 \text{ k}\Omega$$

$$V_{eff} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox}(W/L)}} = 0.205 \text{ V}$$

 So the minimum  $V_{out}$  is then  $2V_{eff} + V_{tn} = 0.98V$ , which is 0.77V larger than the simple current mirror while  $r_{out}$  is increased by 30 times.



Chapter 3 Figure 14


## 3.7 Cascode gain stage

In modern IC design, a commonly used configuration for a single-stage amplifier is a cascode amplifier. This configuration consists of a CS transistor feeding into a CG one. In (a) below, both CS Q1 and cascode transistor Q2 are NMOS (telescopic-cascode amplifier)

In (b), CS Q1 is NMOS and cascode transistor Q2 is PMOS (folded-cascode amplifier).

Two major reasons for cascode stages: (1) they provide large gain when current sources are realized with cascode current mirrors; (2) they limit the voltage across Q1, minimizing short channel effects.

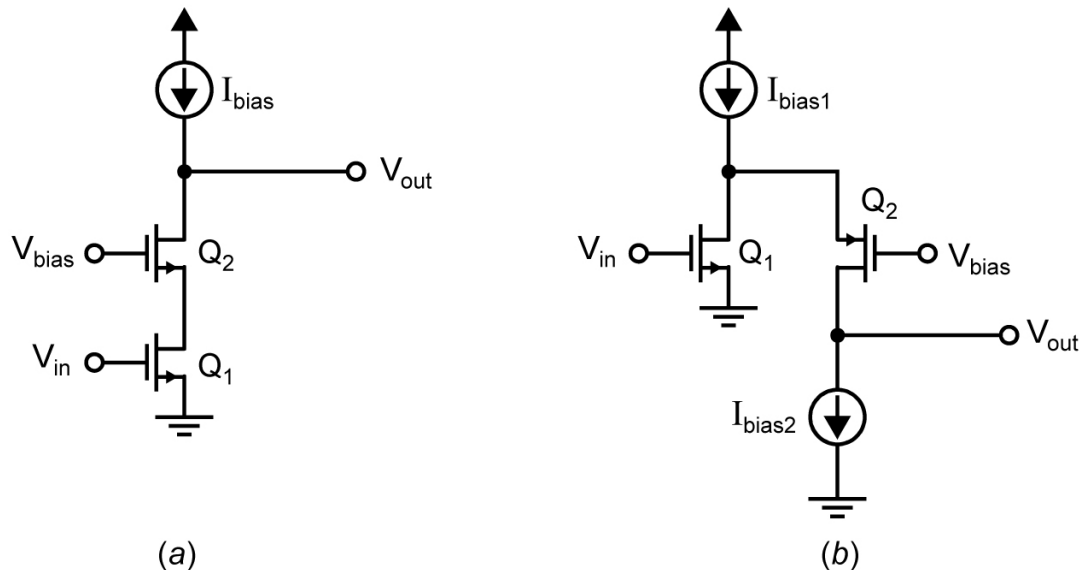The main drawback of cascode stages is that the output voltage swing is reduced in order to keep both Q1 and Q2 in active region when compared to the CS amplifier.



# Small-signal model

The gain from the input to the source of  $Q_2$  is simply that of a common-source amplifier with a load resistance of  $r_{in2}$  and is therefore given by

$$\frac{V_{s2}}{V_{in}} = -g_{m1}(r_{ds1} || r_{in2}) = -\frac{g_{m1}}{g_{ds1} + g_{in2}} \quad (3.52)$$

The impedance looking into source of  $Q_2$

$$g_{in2} = 1/r_{in2} = \frac{g_{m2} + g_{s2} + g_{ds2}}{1 + \frac{R_L}{r_{ds2}}} \cong \frac{g_{m2}}{1 + \frac{R_L}{r_{ds2}}}$$

The gain from the source of  $Q_2$  to the output is simply that derived earlier for the common-gate stage.

$$\begin{aligned} \frac{V_{out}}{V_{s2}} &= \frac{g_{m2} + g_{s2} + g_{ds2}}{g_{ds2} + G_L} \\ &\cong g_{m2}(r_{ds2} || R_L) = \frac{g_{m2}}{(g_{ds2} + G_L)} \end{aligned}$$

The overall gain is


$$A_V = \frac{V_{s2} V_{out}}{V_{in} V_{s2}} \cong -g_{m1} g_{m2} (r_{ds1} || r_{in2}) (r_{ds2} || R_L)$$

The impedance looking into drain of  $Q_2$

$$r_{d2} \cong g_{m2} r_{ds1} r_{ds2}$$

The total output resistance will be

$$R_{out} = r_{d2} || R_L$$

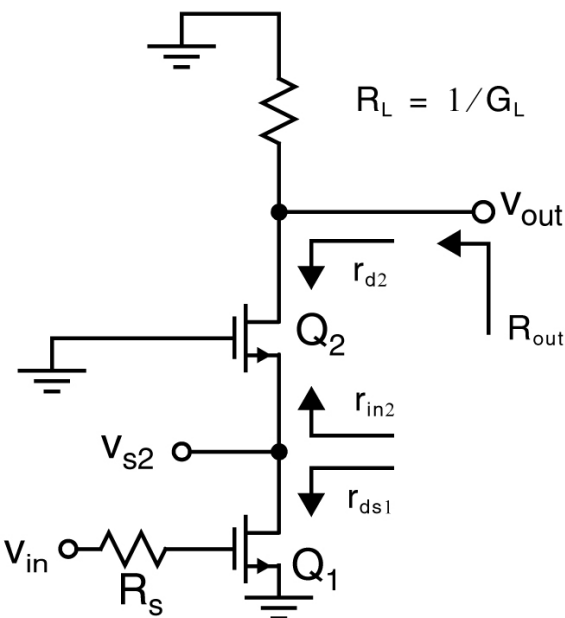

Chapter 3 Figure 16



# Example 3.9 (page 133)

Find approximate expressions for the gain and output resistance of the cascode stage in Fig. 3.15(a) assuming  $I_{bias}$  is a simple current source with an output impedance on the order of  $R_L \approx r_{ds-p}$

Compute approximate numerical results assuming all transistors have  $g_m$  on the order of 0.5mA/V and  $r_{ds}$  on the order of 100k $\Omega$ .

We shall drop the indices for all small-signal values under the assumption that the transistors are somewhat matched and to simplify matters since we are only deriving an approximate answer.

$$g_{in2} \approx \frac{1}{2}g_m \Rightarrow r_{in2} \approx \frac{2}{g_m}$$


Assuming  $r_{ds1}$  is much larger than  $r_{in2}$ , the gain

$$\frac{v_{s2}}{v_{in}} \approx -\frac{g_m}{g_m/2} = -2$$

$$\frac{v_{out}}{v_{s2}} \approx \frac{1}{2}g_m r_{ds}$$

$$A_V = \frac{v_{s2}}{v_{in}} \cdot \frac{v_{out}}{v_{s2}} \approx -g_m r_{ds}$$

 Since  $R_L \ll r_{d2}$ , the output resistance is  $R_{out} \approx r_{ds}$



Chapter 3 Figure 16

The gain in this case is only a factor of 2 larger than that for a common-source amplifier.


Also, almost all of the gain is across Q2.

# Example 3.10 revised (page 135)

Find approximate expressions for the gain and output resistance of the cascode stage in Fig. 3.15(a) assuming  $I_{bias}$  is a simple current source with an output impedance on the order of  $R_L \approx g_{m-p} r_{ds-p}^2 \approx g_m r_{ds}^2$

Compute approximate numerical results assuming all transistors have  $g_m$  on the order of 0.5mA/V and  $r_{ds}$  on the order of 100k $\Omega$ .

 We shall drop the indices for all small-signal values under the assumption that the transistors are somewhat matched and to simplify matters since we are only deriving an approximate answer.



Chapter 3 Figure 16

$$g_{in2} = 1/r_{in2} \approx \frac{g_m}{1 + g_{ds} g_m r_{ds}^2} \cong g_{ds}$$

$$\Rightarrow r_{in2} \approx r_{ds}$$

$$\frac{v_{s2}}{v_{in}} \approx -\frac{1}{2} g_m r_{ds}$$

$$\text{since } R_L \gg r_{ds2}, \quad \frac{v_{out}}{v_{s2}} \approx g_m r_{ds}$$

$$A_V \approx -\frac{1}{2} g_m^2 r_{ds}^2 = -\frac{1}{2} \left( \frac{g_m}{g_{ds}} \right)^2$$


$$R_{out} = R_L || r_{d2} \approx \frac{1}{2} g_m r_{ds}^2$$

The gain and output resistance is dramatically improved compared to the previous example when a cascode current mirror is used for  $I_{bias}$ .
 
## 3.8 Differential pair and gain stage

A differential pair have identically-sized and –biased transistors  $Q_1$  and  $Q_2$ .

It is usually used as the input stage of a Operational Amplifier.



# Small-signal model using T model

To simplify the analysis, we ignore the output impedance of the transistors temporarily.

Defining the differential input voltage as  $v_{in} \equiv v^+ - v^-$ ,

$$i_{d1} = i_{s1} = \frac{v_{in}}{r_{s1} + r_{s2}} = \frac{v_{in}}{1/g_{m1} + 1/g_{m2}}$$

Since both  $Q_1$  and  $Q_2$  have the same bias currents,  $g_{m1} = g_{m2}$ .


$$i_{d1} = \frac{g_{m1} v_{in}}{2}$$

Also, since  $i_{d2} = i_{s2} = -i_{d1}$ ,

$$i_{d2} = -\frac{g_{m1} v_{in}}{2}$$

Finally, defining a differential output current,  $i_{out} \equiv i_{d1} - i_{d2}$ , the following relationship is obtained:

$$i_{out} = g_{m1} v_{in}$$

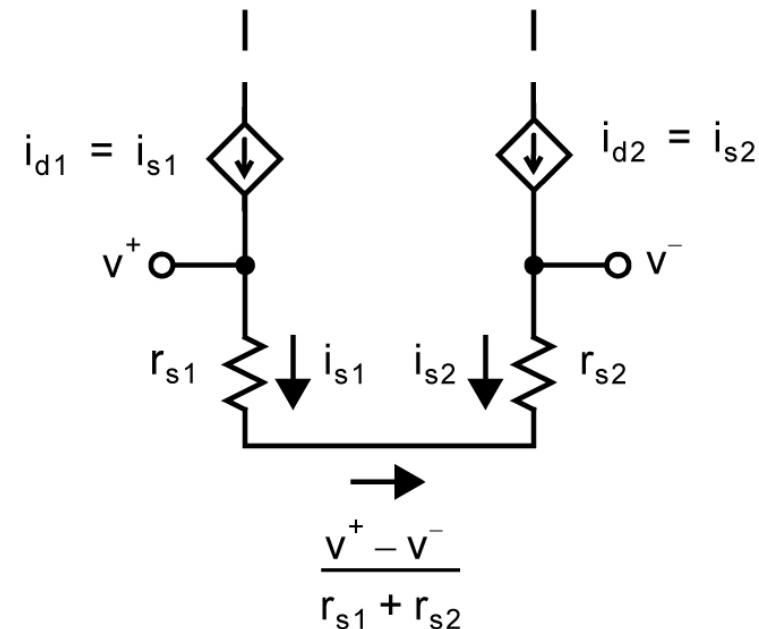


Chapter 3 Figure 18

# Differential pair with resistive load

If two resistive loads  $R_L$  are connected between the drains of  $Q_1$  and  $Q_2$  and a positive supply, the result is a differential output voltage between the two drain nodes,  $v_{out} = (g_{m1}R_L)v_{in}$  and the stage has a differential small-signal gain of  $g_{m1}R_L$ .

Note that  $r_{ds}$  is neglected.

 

# Differential pair with current mirror

As with the CS amplifier, we can replace the resistor by current mirrors as an active load. Then, a complete differential-input, single-ended output gain stage can be realized. This circuit is typically the first gain stage in a classical two-stage integrated OpAmp to be discussed later.

From small-signal analysis of the differential pair,


$$i_{d1} = i_{s1} = \frac{g_{m1}}{2} v_{in}$$

$$i_{d4} = i_{d3} = -i_{s1}$$

$$i_{d2} = -i_{s1}$$

$$v_{out} = (-i_{d2} - i_{d4})r_{out} = 2i_{s1}r_{out} = g_{m1}r_{out}v_{in}$$

 How to determine the small-signal output resistance  $r_{out}$ ?



Chapter 3 Figure 19

# Computing $r_{out}$

T model was used for Q1, Q2 and diode-connected Q3 was replaced by an equivalent resistance and hybrid-pi model for Q4.

$$i_x = i_{x1} + i_{x2} + i_{x3} + i_{x4}$$


$$i_{x1} = \frac{V_x}{r_{ds4}}$$

Then assuming the effect of  $r_{ds1}$  can be ignored (since it is much larger than  $r_{s1}$ ), then

$$i_{x2} \cong \frac{V_x}{r_{ds2} + (r_{s1} \parallel r_{s2})} \cong \frac{V_x}{r_{ds2}} \quad \text{since } r_{ds2} \text{ is typically much greater than } r_{s1} \parallel r_{s2}.$$

This  $i_{x2}$  current splits equally between  $i_{s1}$  and  $i_{s2}$  (assuming  $r_{s1} = r_{s2}$  and once again ignoring  $r_{ds1}$ ),
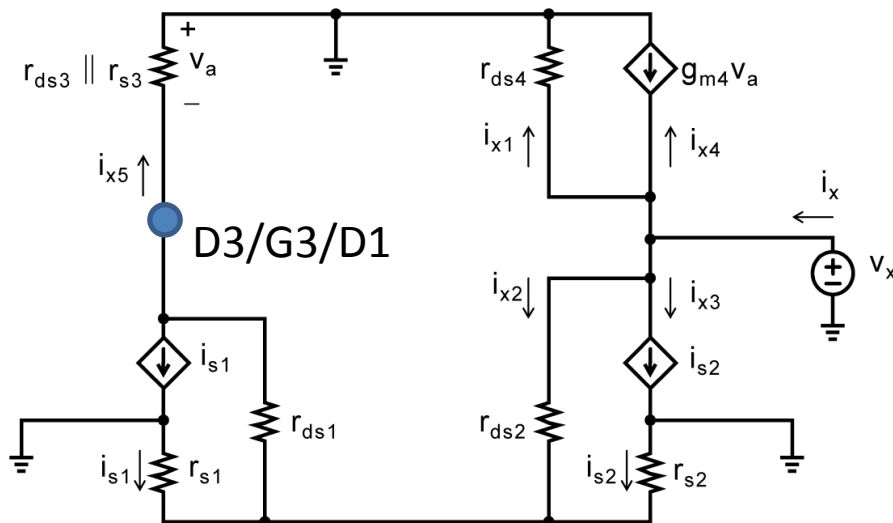
$$i_{s1} = i_{s2} = \frac{-V_x}{2r_{ds2}}$$



# Computing $r_{out}$


However, since the current mirror realized by  $Q_3$  and  $Q_4$  results in  $i_{x4} = i_{x5}$  (assuming  $g_{m4} = 1/r_{s4} = 1/r_{s3}$  and  $r_{ds3}$  is much larger than  $r_{s3}$ ), the current  $i_{x4}$  is given by

$$i_{x4} = -i_{s1} = -i_{s2} = -i_{x3}$$

$$r_{out} = \frac{v_x}{i_{x1} + i_{x2} + i_{x3} + i_{x4}} = \frac{v_x}{(v_x/r_{ds4}) + (v_x/r_{ds2})}$$

$$r_{out} = r_{ds2} \parallel r_{ds4}$$
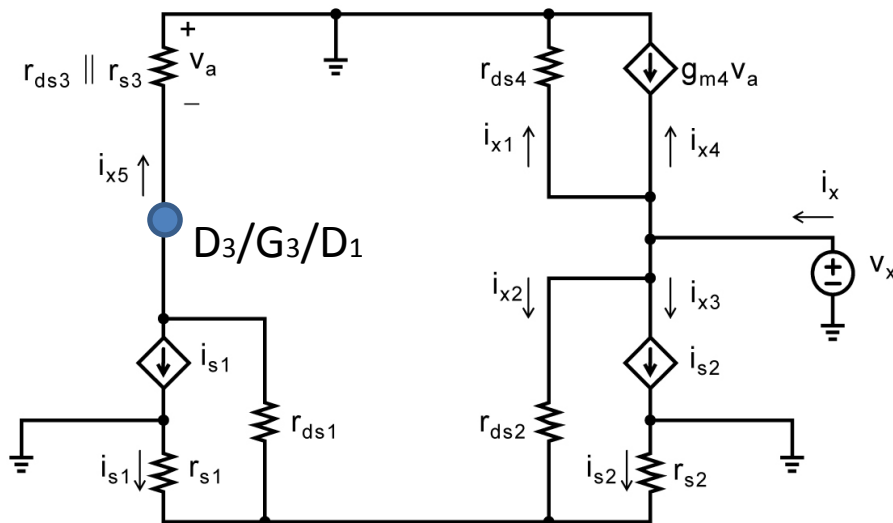
$$A_v = g_{m1}(r_{ds2} \parallel r_{ds4})$$



Chapter 3 Figure 20