

Digital Integrated Circuits

A Design Perspective

Jan M. Rabaey
Anantha Chandrakasan
Borivoje Nikolic


The Inverter

Revised from Digital Integrated Circuits, © Jan M. Rabaey et al, 2003




Propagation Delay


CMOS Inverter Propagation Delay

 
 
$$t_{pHL} = f(R_{on} \cdot C_L)$$
$$= 0.69 R_{on} C_L$$





MOS transistor model for simulation

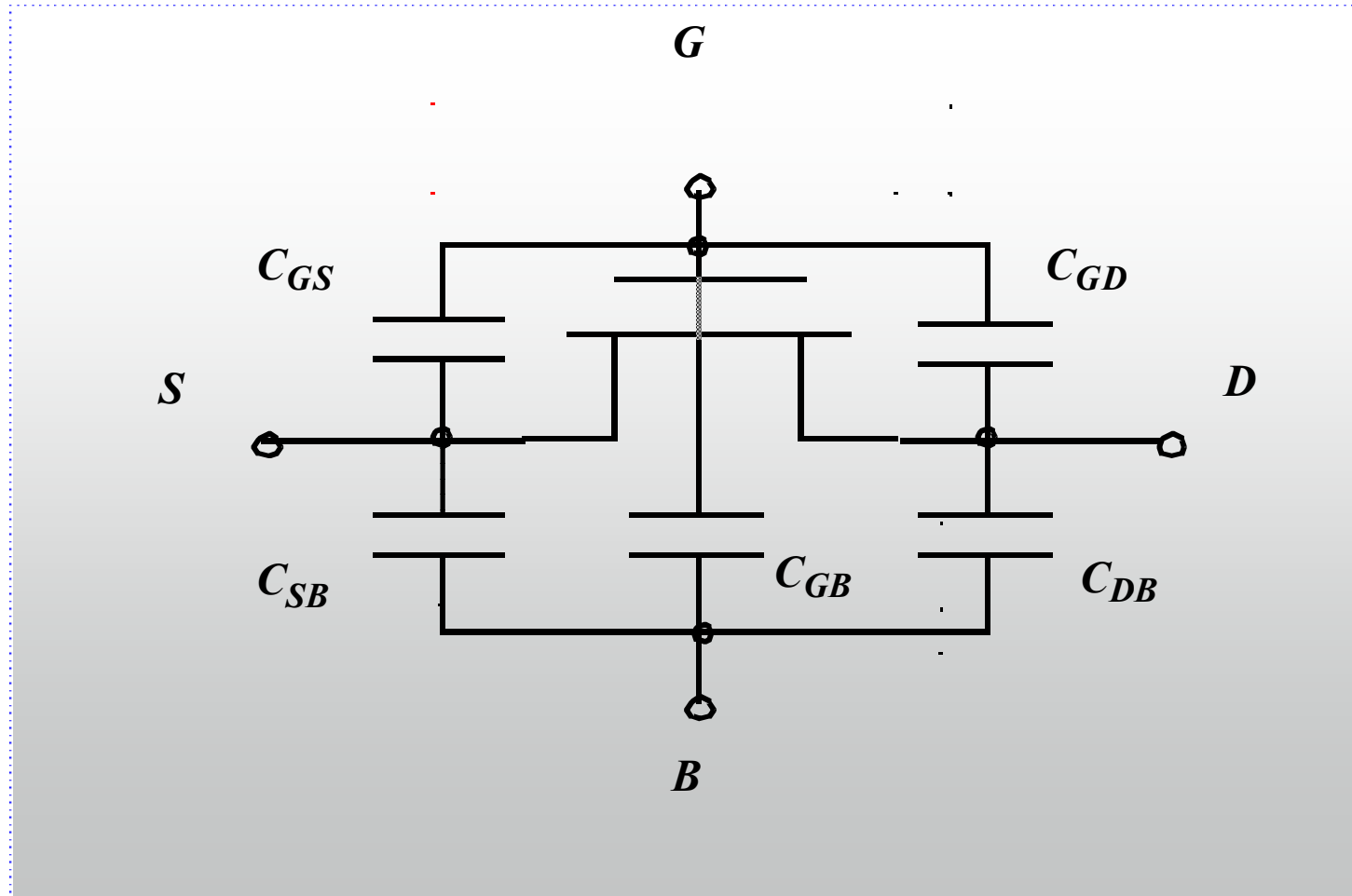


Computing the Capacitances

 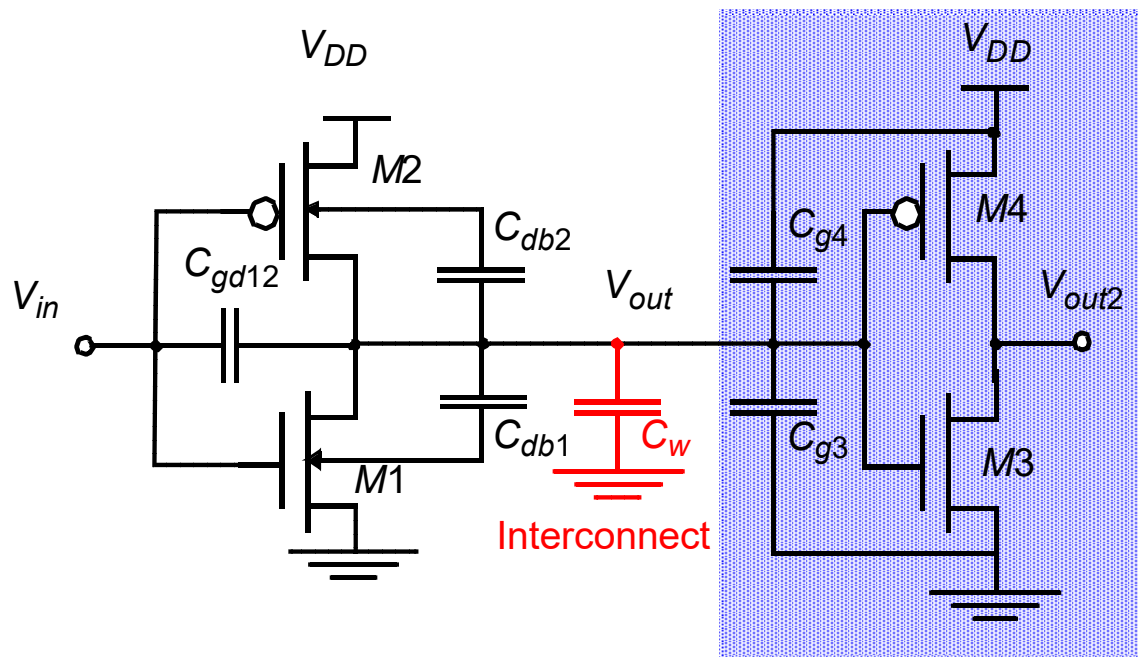Consider each capacitor individually is almost impossible for manual analysis. What capacitors count in C_L ?



Simplified Model

 


Computing the Capacitances

- ❑ NMOS and PMOS transistor are either in **cutoff** or **saturation** mode during at least the first half (50%) of the output transient.
- ❑ So, the only contributions to C_{gd} are the overlap capacitance, since channel capacitance occurs between either **Gate-Body** for transistors in cutoff region or **Gate-Source** for transistors in saturation region.

The Miller Effect


 
The lumped capacitor model requires the floating C_{gd1} capacitor be replaced by a capacitor to GND using Miller effect.



“A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.”

The Miller Effect

  - ❑ Consider the situation that an impedance is connected between *input* and *output* of an amplifier



- The same current flows from (out) the top input terminal if an impedance $Z_{in, Miller}$ is connected across the input terminals
- The same current flows to (in) the top output terminal if an impedance $Z_{out, Miller}$ is connected across the output terminal
- This is known as Miller Effect
- Two important notes to apply Miller Effect:
 - ✓ There should be a common terminal for input and output
 - ✓ The gain in the Miller Effect is the gain after connecting feedback impedance Z_f

Computing the Capacitances


Capacitor	Expression
C_{gd1}	$2 C_{GD0} W_n$
C_{gd2}	$2 C_{GD0} W_p$
C_{db1}	$K_{eqn} (AD_n CJ + PD_n CJSW)$
C_{db2}	$K_{eqp} (AD_p CJ + PD_p CJSW)$
C_{g3}	$C_{ox} W_n L_n$
C_{g4}	$C_{ox} W_p L_p$
C_w	From Extraction
C_L	Σ

The capacitance between drain and bulk, C_{db1} and C_{db2} , are due to the reverse-biased pn-junction.

Such a capacitor is, unfortunately, quite nonlinear and depends heavily on the applied voltage.

In Chapter 3 we replaced the nonlinear capacitor by a linear one with the same change in charge for the voltage range of interest. A multiplication factor, K_{eq} , is introduced to relate the linearized capacitor to the value of the junction capacitance under zero-bias conditions (usually in the range of 0.6 to 0.9).

Junction Capacitance

 

$$C_j = \frac{C_{j0}}{(1 - V_D / \phi_0)^m}$$

$m = 0.5$: abrupt junction
 $m = 0.33$: linear junction

Linearizing the Junction Capacitance

Replace non-linear capacitance by
large-signal equivalent linear capacitance
which displaces equal charge
over voltage swing of interest

$$C_{eq} = \frac{\Delta Q_j}{\Delta V_D} = \frac{Q_j(V_{high}) - Q_j(V_{low})}{V_{high} - V_{low}} = K_{eq} C_{j0}$$

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} [(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}]$$

 


Table 6: Contact to Active

Rule	Description	Lambda
6.1	Exact contact size	2 x 2
6.2	Minimum active overlap	1.5
6.3	Minimum contact spacing	3
6.4	Minimum spacing to gate of transistor	2

 


Table 7: Metal1

Rule	Description	Lambda
7.1	Minimum width	3
7.2	Minimum spacing	3
7.3	Minimum overlap of any contact	1


 



Table 3: Poly

Rule	Description	Lambda
3.1	Minimum width	2
3.2	Minimum spacing	3
3.2.a	Minimum spacing over active	3
3.3	Minimum gate extension of active	2
3.4	Minimum active extension of poly	3
3.5	Minimum field poly to active	1

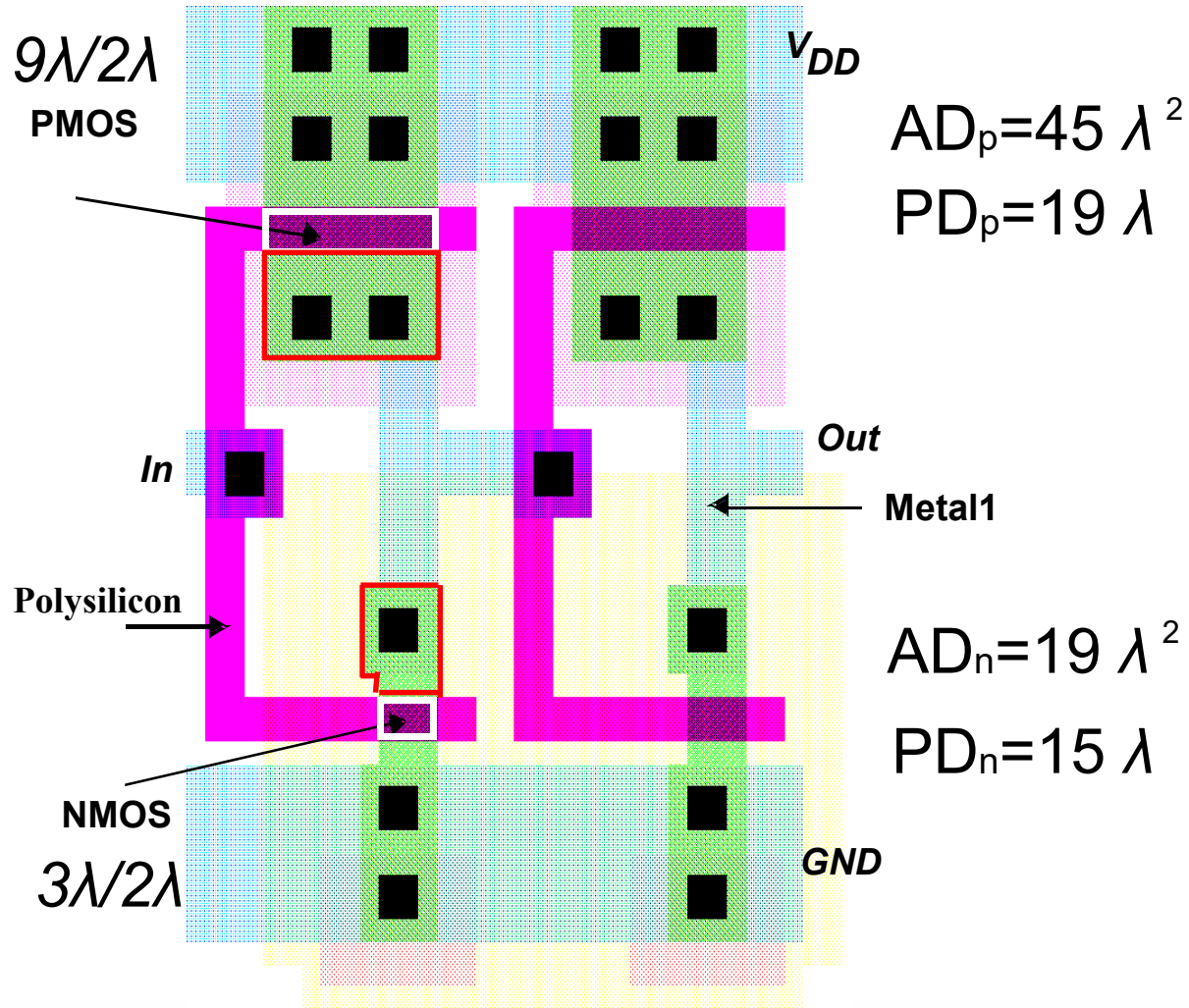

Inverter

Junction Capacitance L_s (from Ch. 3)

 

Junction capacitance per unit length

$$C_{diff} = C_{bottom} + C_{sw} = C_j \times AREA + C_{jsw} \times PERIMETER$$

$$= C_j L_s W + C_{jsw} (2L_s + W)$$

Junction capacitance per unit area

Computation of all capacitors

	C_{ox} (fF/ μm^2)	C_o (fF/ μm)	C_j (fF/ μm^2)	m_j	ϕ_b (V)	C_{jsw} (fF/ μm)	m_{jsw}	ϕ_{bSW} (V)
NMOS	6	0.31	2	0.5	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9


Table 5.2 Components of C_L (for high-to-low and low-to-high transitions).

Capacitor	Expression	Value (fF) (H→L)	Value (fF) (L→H)	
C_{gd1}	$2 CGD0_n W_n$	0.23	0.23	Intrinsic
C_{gd2}	$2 CGD0_p W_p$	0.61	0.61	
C_{db1}	$K_{eqn} AD_n CJ + K_{eqsw n} PD_n CJSW$	0.66	0.90	
C_{db2}	$K_{eqp} AD_p CJ + K_{eqsw p} PD_p CJSW$	1.5	1.15	
C_{g3}	$(CGD0_n + CGSO_n) W_n + C_{ox} W_n L_n$	0.76	0.76	Extrinsic
C_{g4}	$(CGD0_p + CGSO_p) W_p + C_{ox} W_p L_p$	2.28	2.28	
C_w	From Extraction	0.12	0.12	
C_L	Σ	6.1	6.0	

C_{db} will be **slightly** different in L-to-H and H-to-L, why? (the pn junction reverse bias voltage range)

Transient Response

 C_{gd} directly couples the steep input change before the circuit can even start to react to the changes at input (potential forward bias the pn junction)



Low-to-High and High-to-Low delay

- It is desired to have identical propagation delays for both rising and falling inputs.
- Equal delay requires equal equivalent on-resistance, thus equal current I_{DAST} (neglecting the channel length modulation)
- This demands almost the same requirements for a V_m at $V_{DD}/2$. Why?


Requirements for equal delay

$$I_{DSAT} = k' \frac{W}{L} \left((V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

$$I_{Dn} = k_n' \left(\frac{W}{L} \right)_n V_{DSATn} \left((V_{DD} - V_{Tn}) - \frac{V_{DSATn}}{2} \right)$$

$$I_{Dp} = k_p' \left(\frac{W}{L} \right)_p V_{DSATp} \left((V_{DD} - V_{Tp}) - \frac{V_{DSATp}}{2} \right)$$

Assume $V_{DD} \gg V_{Tp} + V_{DSATp} / 2$
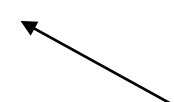
$$\text{then } \frac{k_p' V_{DSATp} (W / L)_p}{k_n' V_{DSATn} (W / L)_n} = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = 1$$


This is exactly the formerly defined parameter r (last lecture)

Design for delay performance


- ❑ Keep capacitances small
 - careful layout, e.g. to keep drain diffusion as small as possible

- ❑ Increase transistor sizes
 - watch out for self-loading! When intrinsic capacitance starts to dominate the extrinsic ones

- ❑ Increase V_{DD} (????)


Delay as a function of V_{DD}
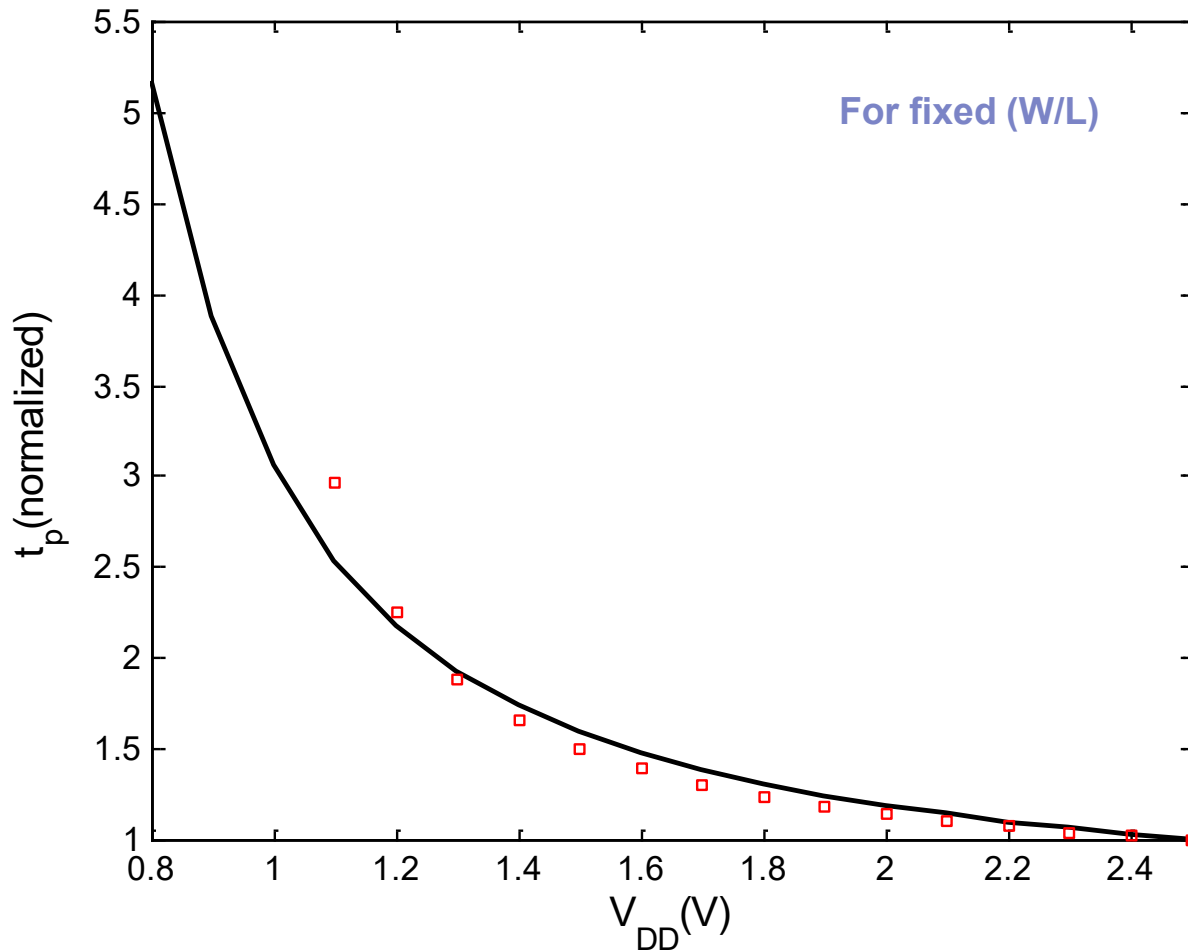
$$t_{pHL} = 0.69 \frac{3C_L V_{DD}}{4 I_{DSATn}} = 0.52 \frac{C_L V_{DD}}{(W/L)_n k'_n V_{DSATn} (V_{DD} - V_{Tn} - V_{DSATn}/2)}$$




Recall a range of low voltage is able to give even better voltage transfer characteristic

Device Sizing

 

Self-loading effect:
Intrinsic capacitances
dominate

NMOS/PMOS ratio

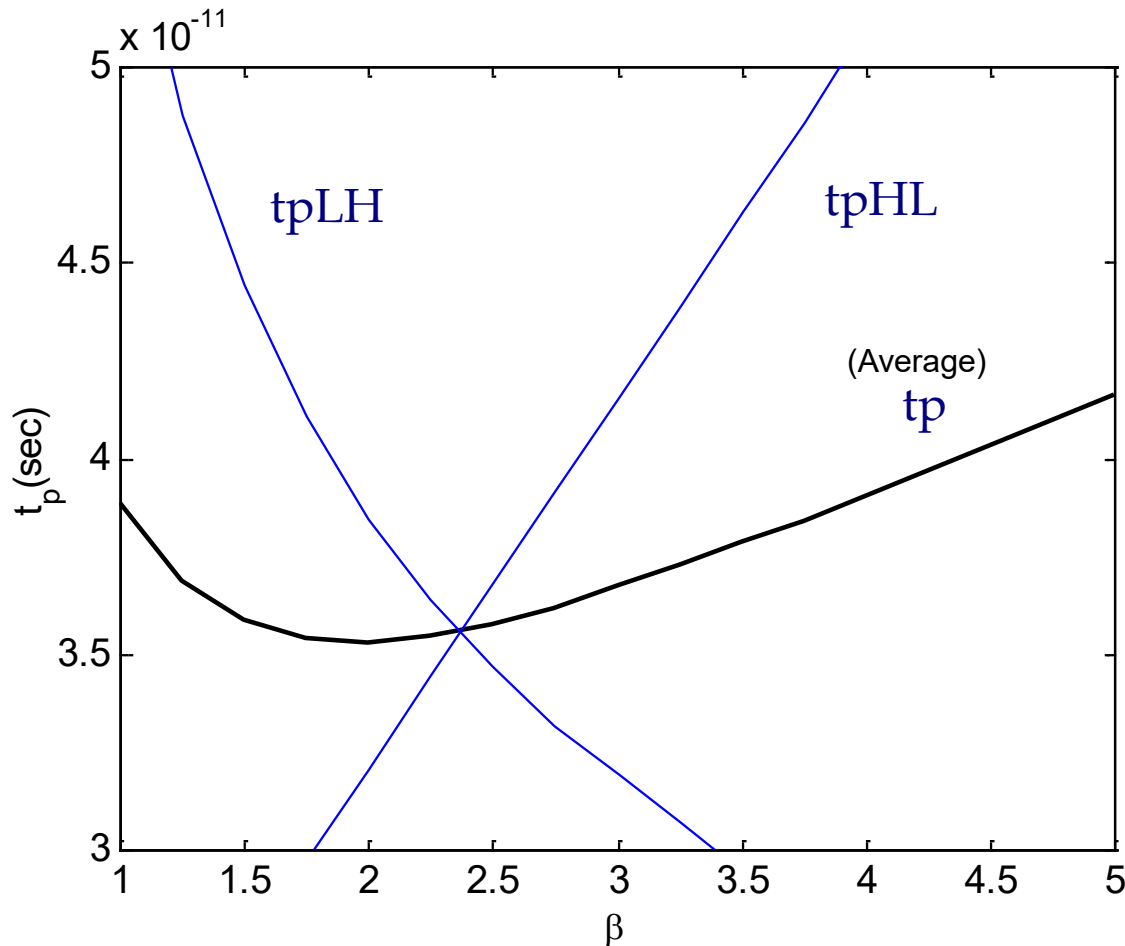


$$\beta = W_p/W_n$$

$$L_p = L_n$$


Widening PMOS improves the L-H delay by increasing the charge current, but it also degrades the H-L by giving a larger parasitic capacitance.

Considering average is more meaningful!!

Delay Definitions

 

Impact of Rise Time on Delay

 


$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r/2)^2}$$



***Custom design
process:
An inverter design
example***


1. Schematic design

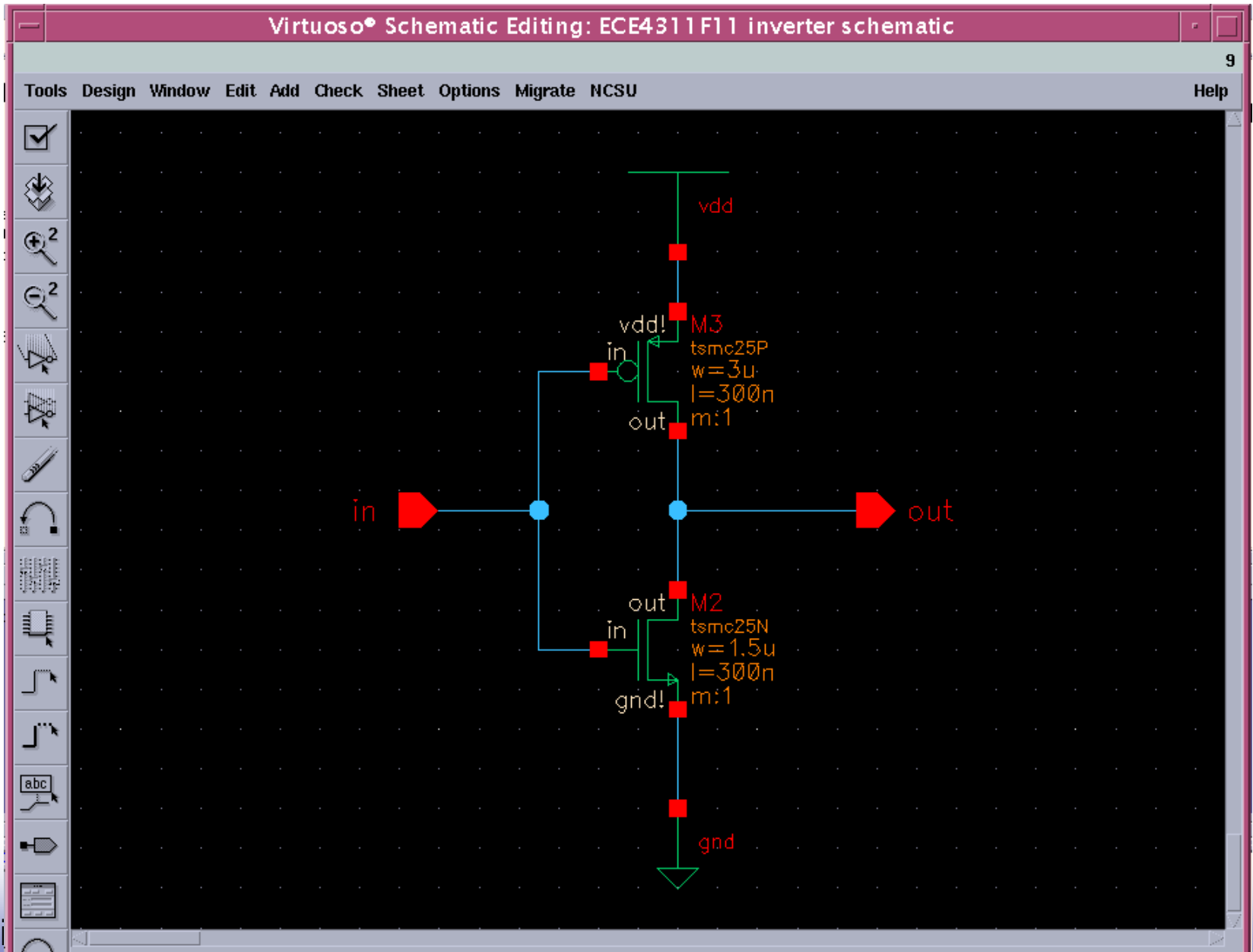


2. Layout design




Step 1: define Nwell (for PMOS)

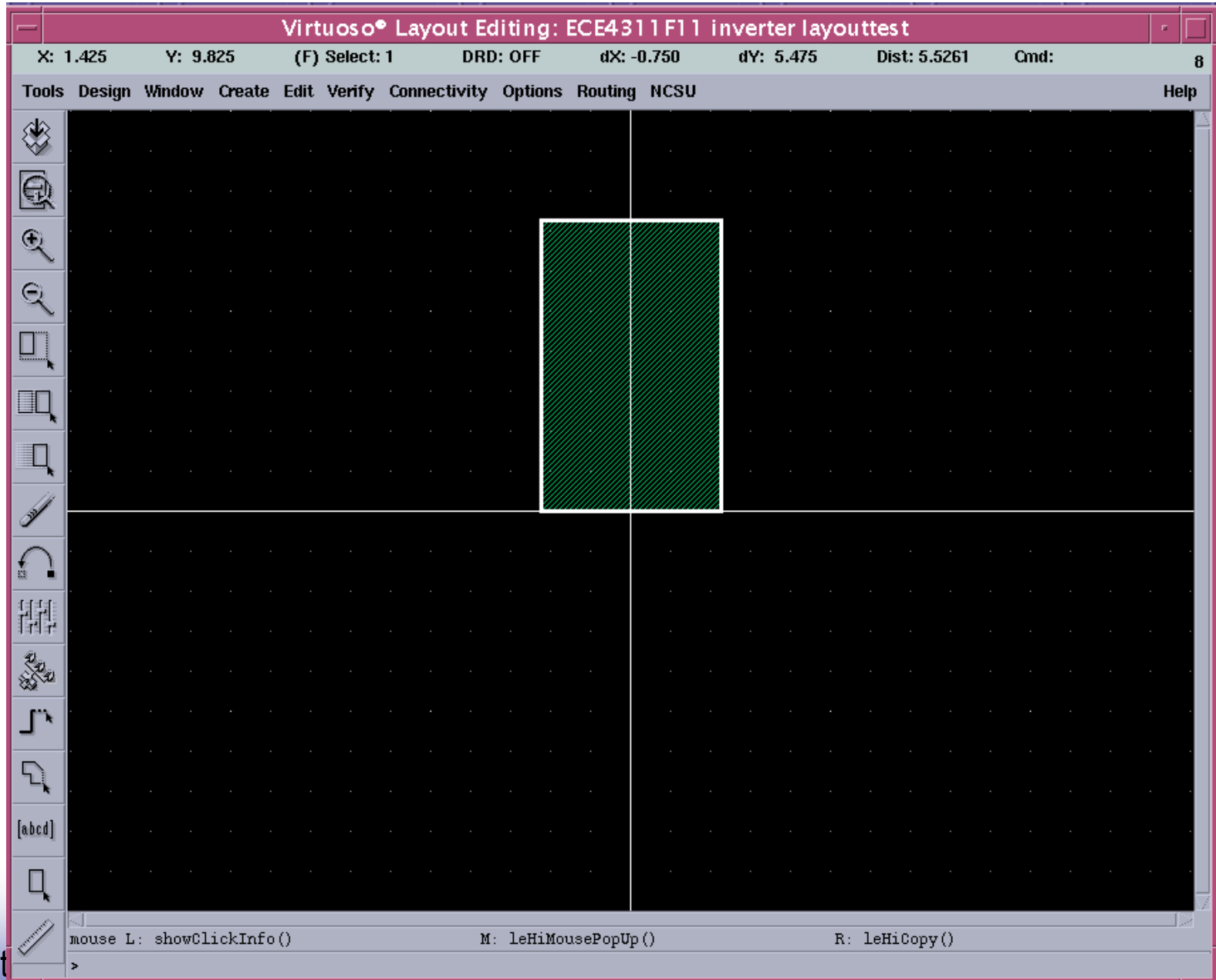

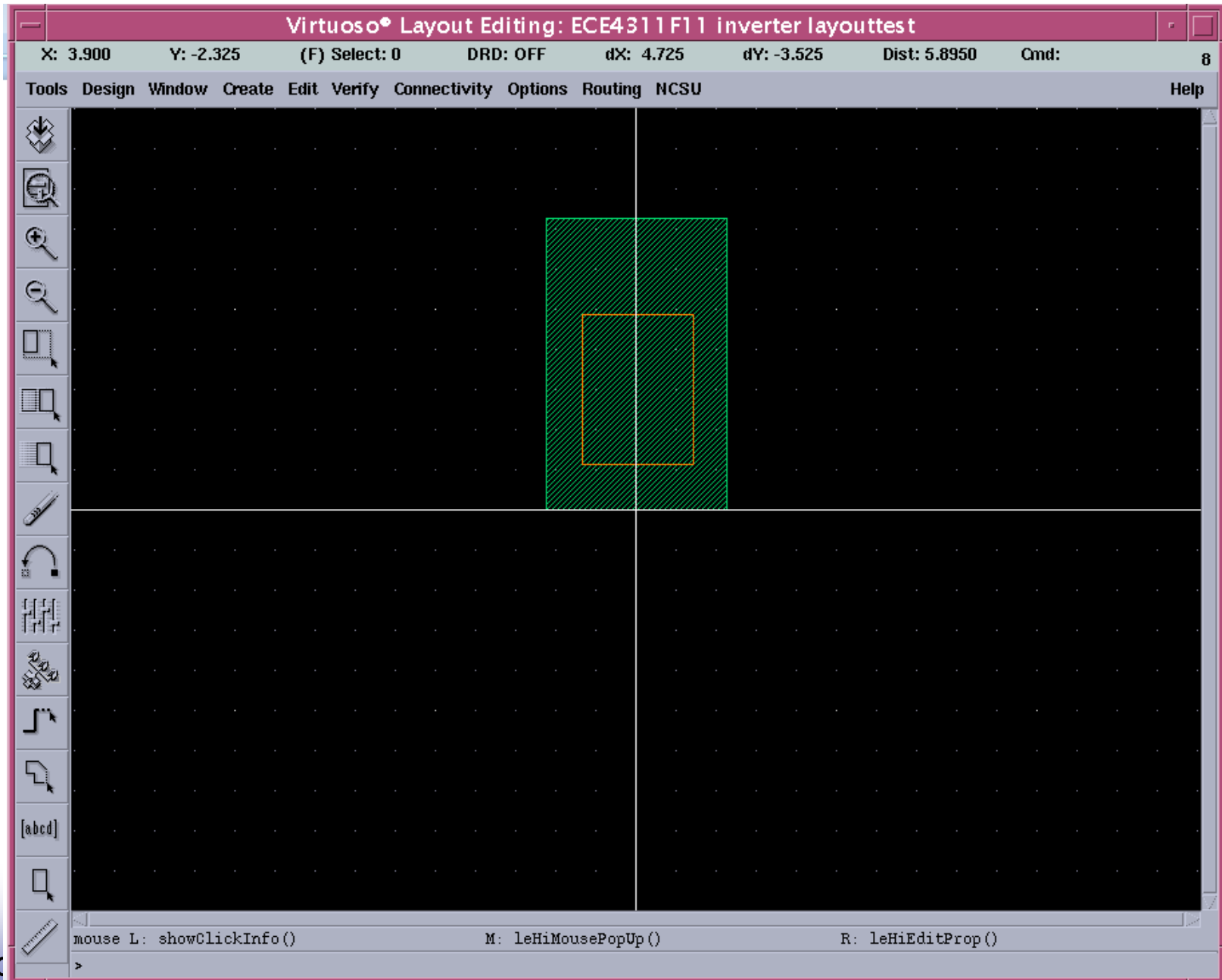
Step 2: define pselect (for PMOS location)




Step 3: define active region (for PMOS)

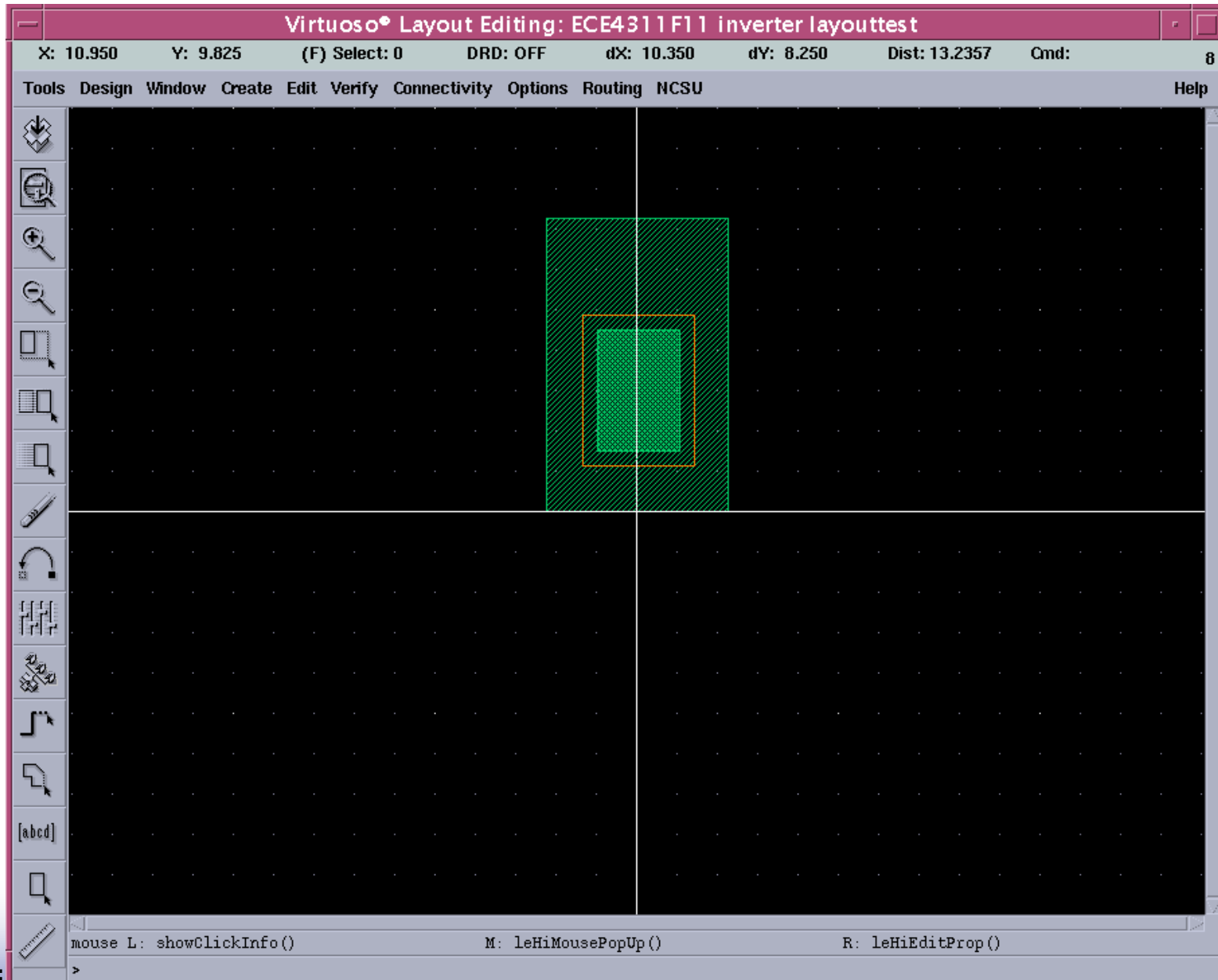


Step 4: define poly (gate for PMOS)

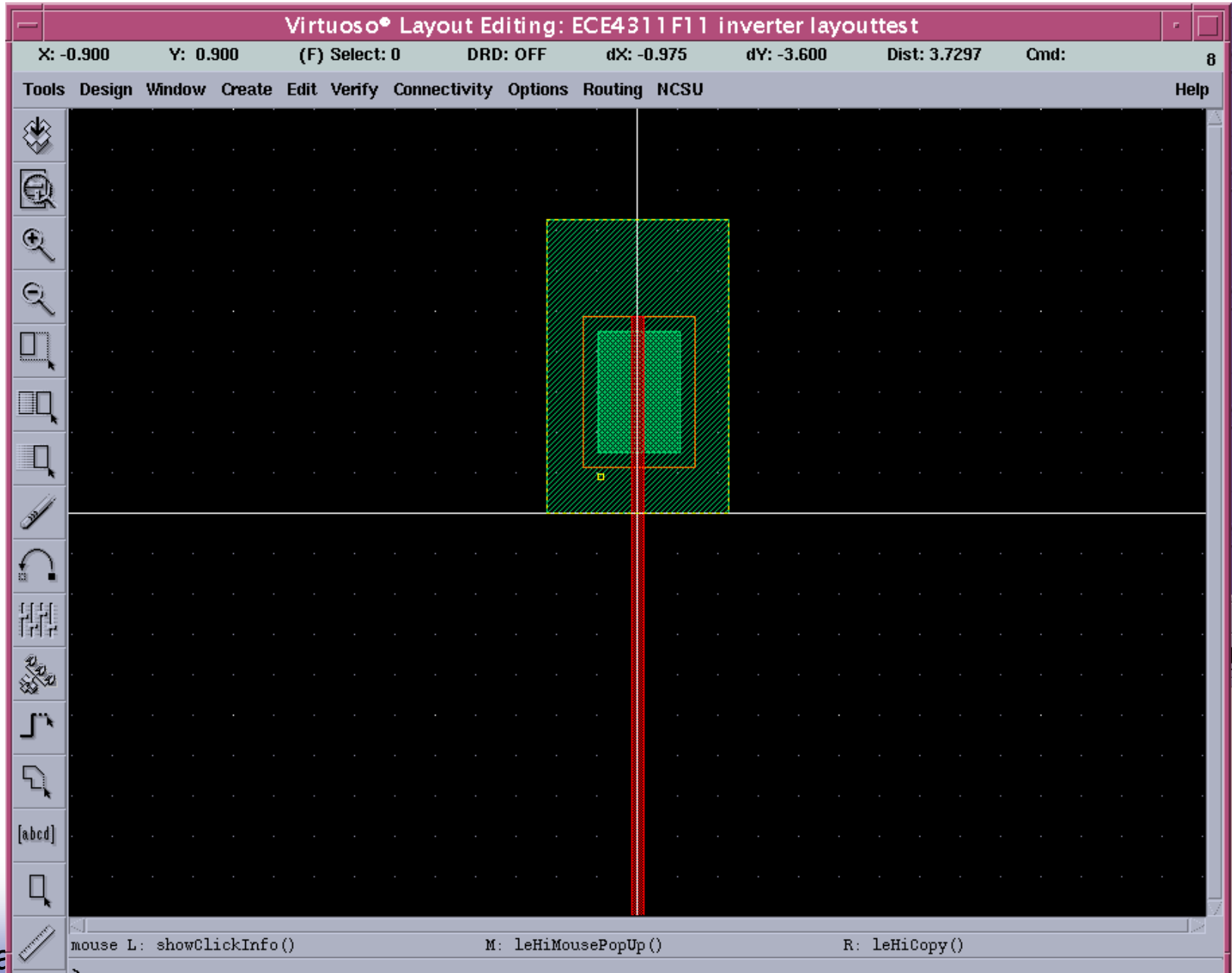


Step 5: define contacts (for PMOS)

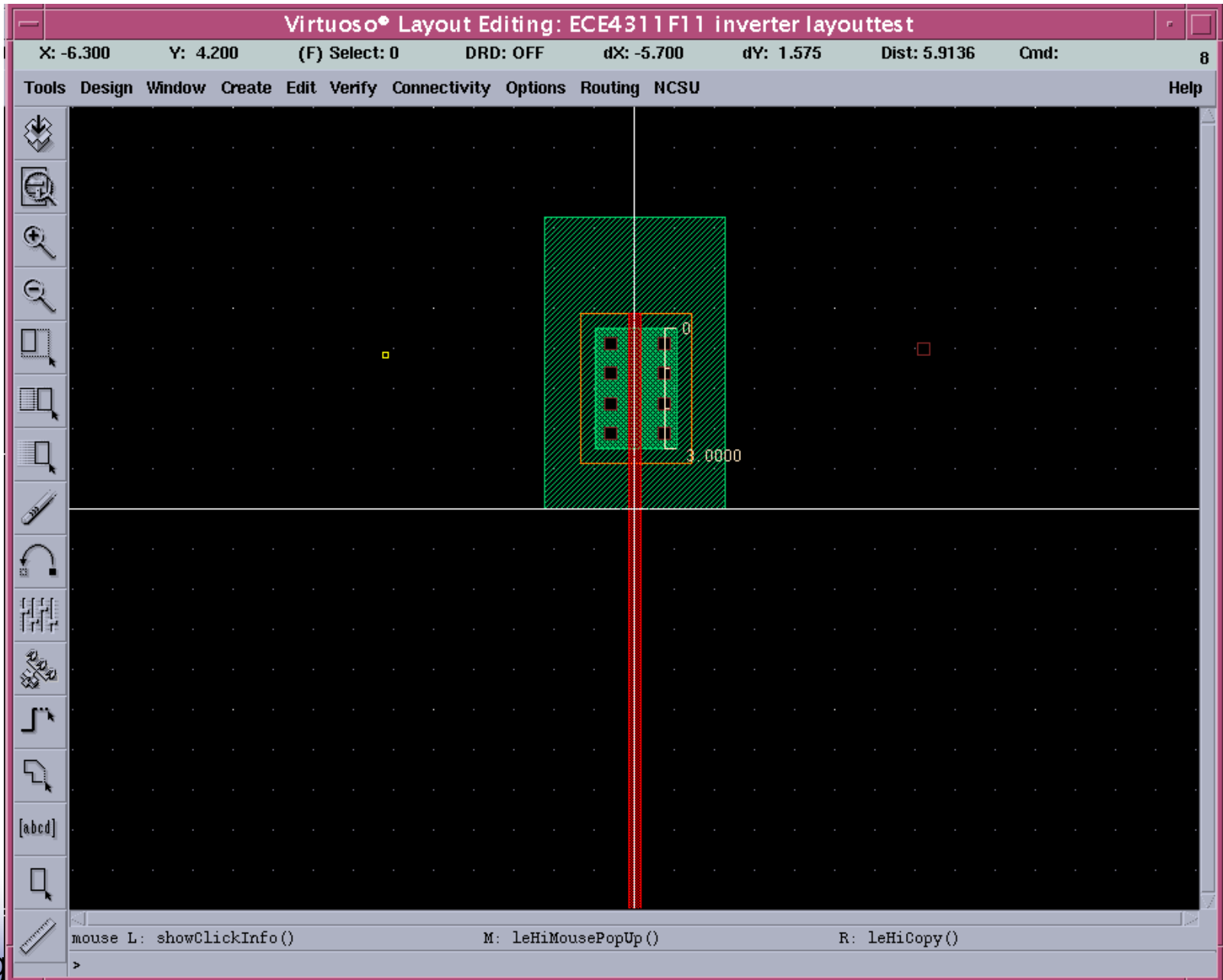

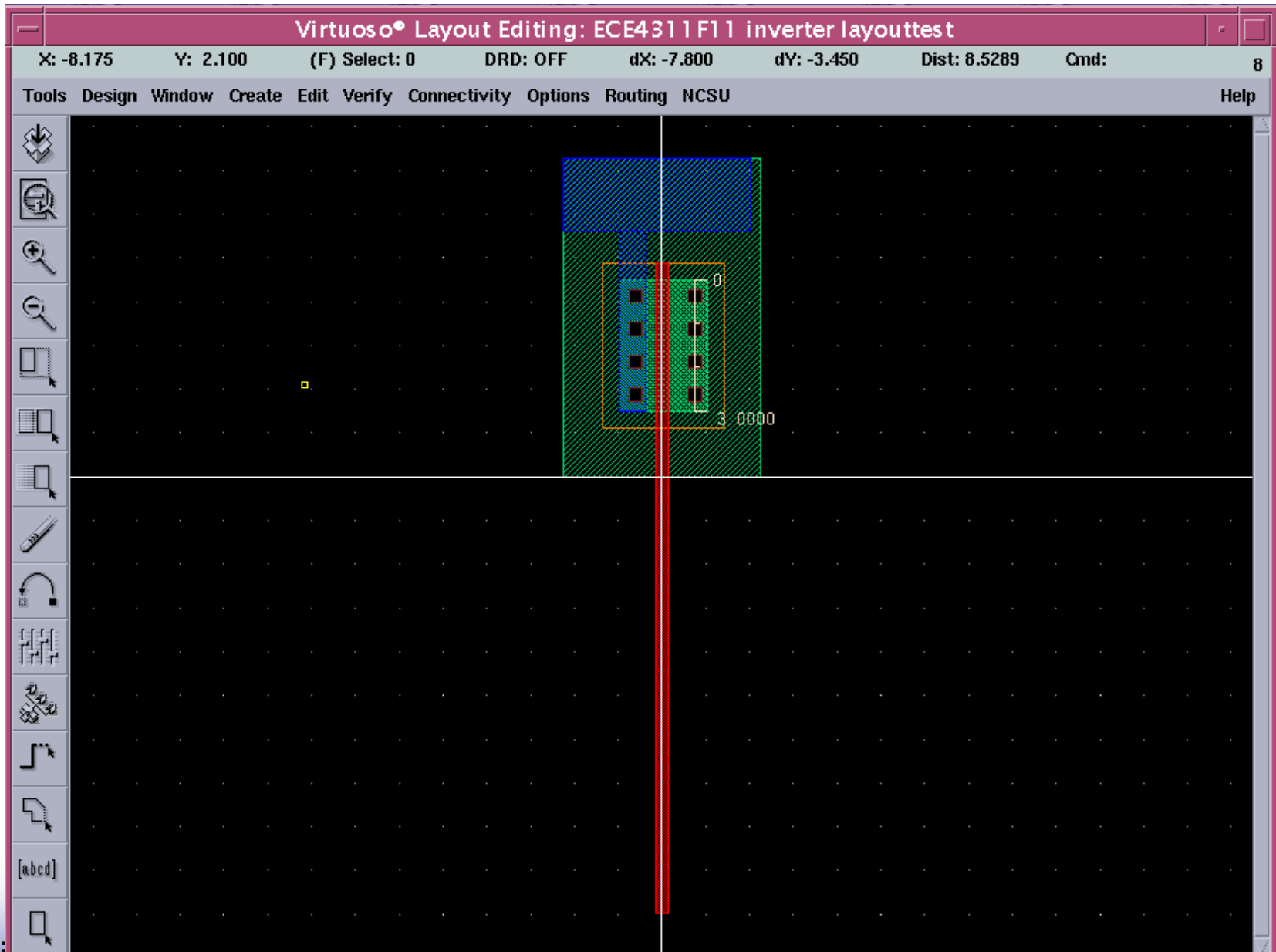
Step 6: define Vdd and connect source (of PMOS) to it




Step 7: make at least one Nwell contact

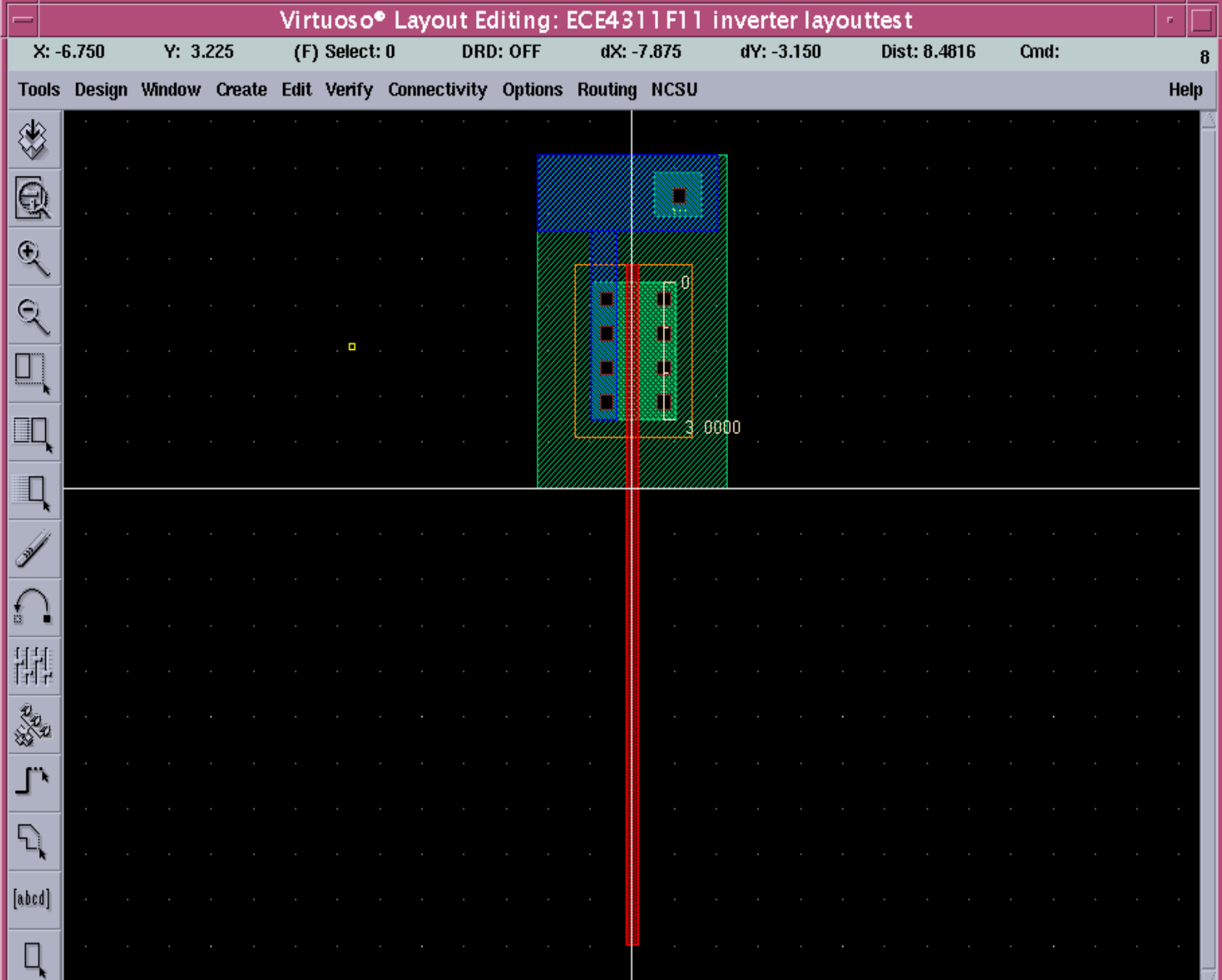

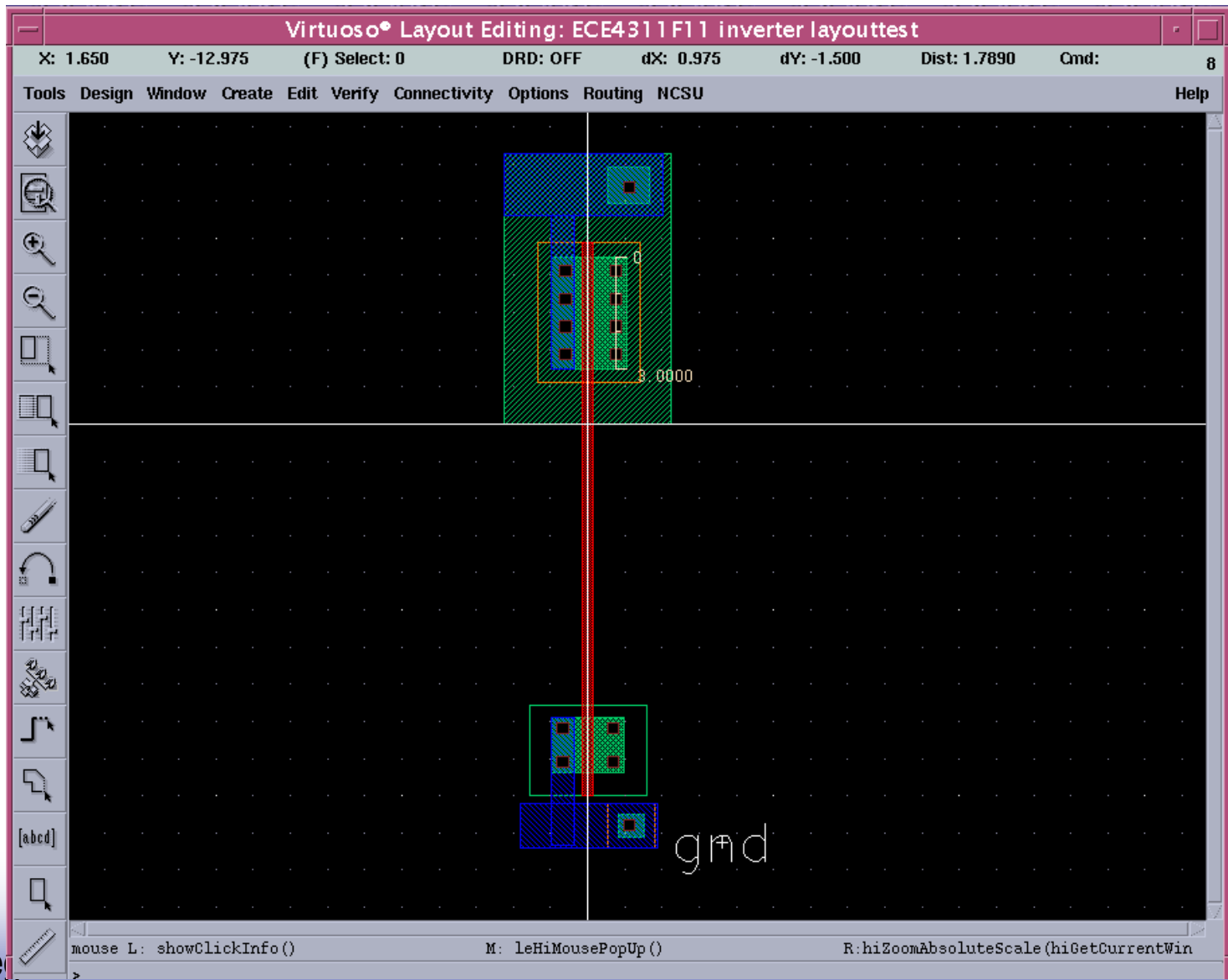Step 8: create NMOS (repeat similar steps before except you do not need make Nwell)



step9: make input and output connections

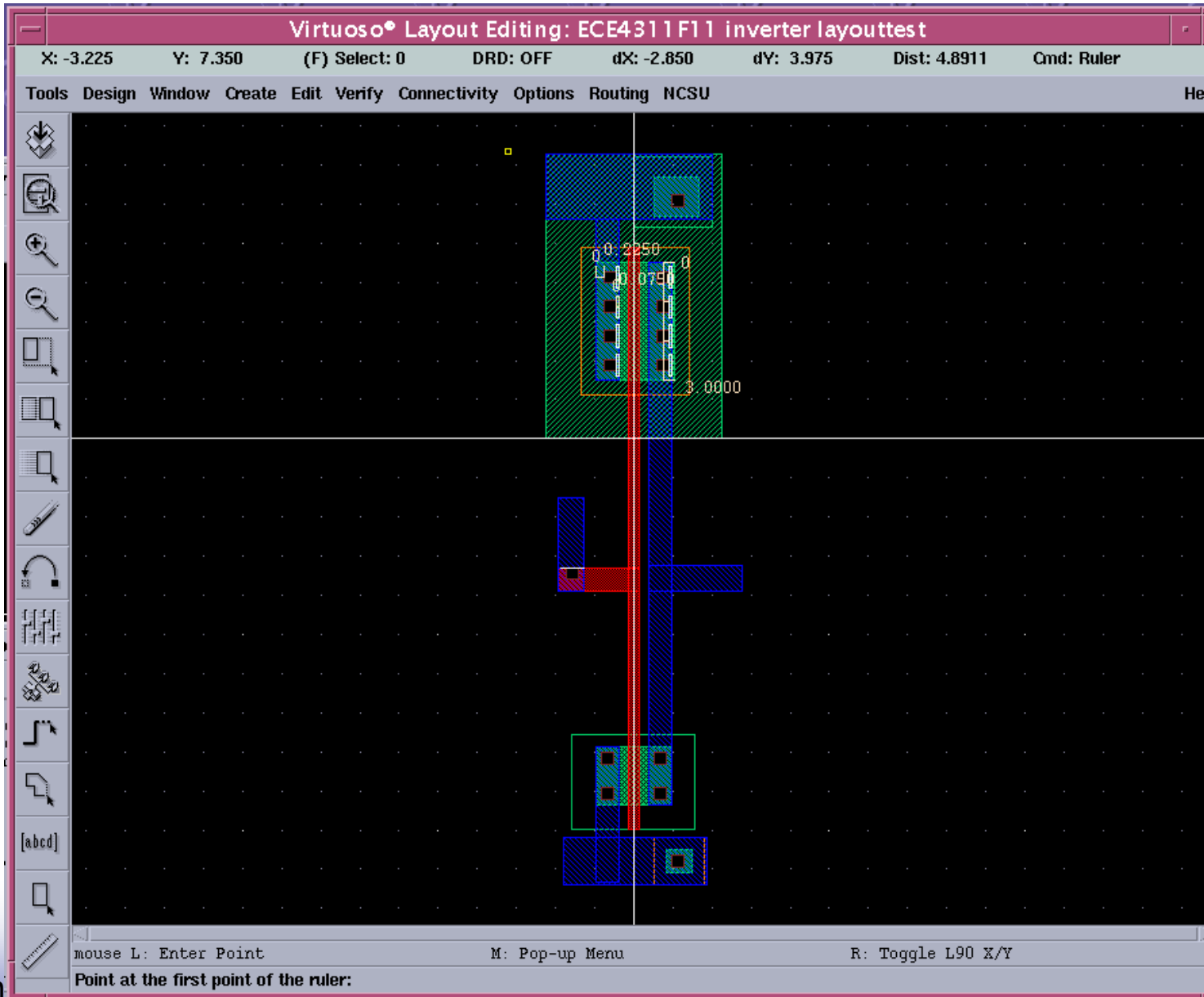


2. DRC (Design Rule Check)


```
icfb - Log: /home/research/thua/CDS.log
File Tools Options Help 1
executing: drc(metalcapCapEdge via4metalcapEdge (enc < (lambda * 3.0)) errMesg)
executing: drc(metalcapCapEdge via4Edge (sep < (lambda * 5.0)) errMesg)
executing: drc(metalcapCapEdge via3Edge (sep < (lambda * 5.0)) errMesg)
executing: saveDerived(geomAnd(metalcap via3) errMesg)
executing: drc(metalcapBottomEdge via4Edge (enc < (lambda * 5.0)) errMesg)
executing: drc(metalcapBottomEdge via3Edge (enc < (lambda * 5.0)) errMesg)
DRC started.....Thu Sep 22 15:53:57 2011
  completed ....Thu Sep 22 15:53:58 2011
  CPU TIME = 00:00:00 TOTAL TIME = 00:00:01
***** Summary of rule violations for cell "inverter layouttest" *****
# errors  Violated Rules
      1  (SCMOS Rule 5.2.b) poly enclosure of contact: 0.15 um
      8  (SCMOS Rule 7.3) metall enclosure of contact: 0.15 um
      9  Total errors found
Found 9 matching marker(s) in view: "inverter".
(SCMOS Rule 7.3) metall enclosure of contact: 0.15 um

mouse L: Enter Point          M: Pop-up Menu          R: Toggle L90 X/Y
Point at the first point of the ruler:
```

Correct error if there is any

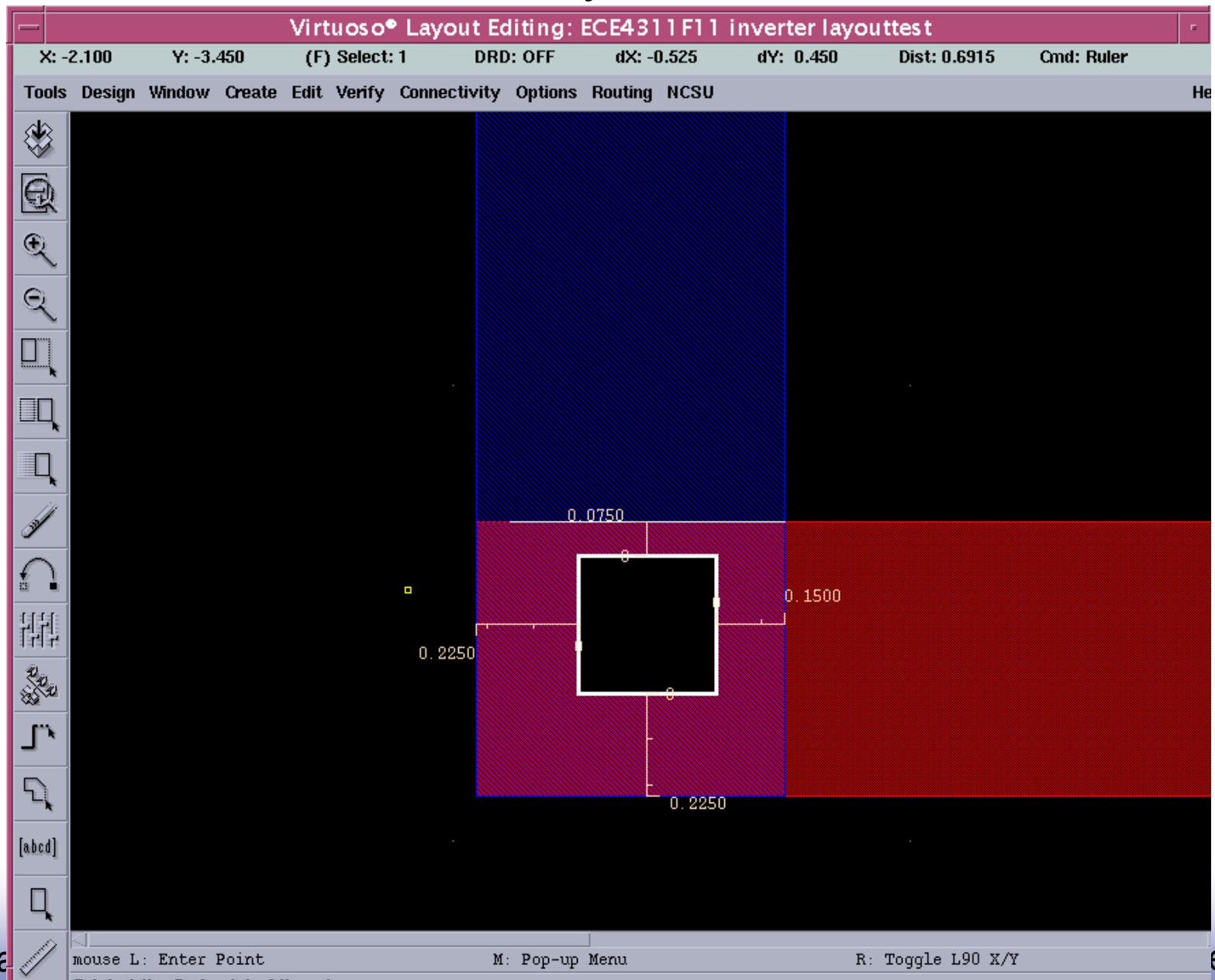

After correction

 

icfb - Log: /home/res

File Tools Options

```
executing: drc(metalcapCapEdge (width < (lambda * 50.0)) errMesg)
drc(metalcapCapEdge (sep < (lambda * 2.0)) errMesg)
drc(metalcapCapEdge (notch < (lambda * 2.0)) errMesg)
executing: saveDerived(geomAndNot(metalcap metal4) errMesg)
executing: drc(metalcapBottomEdge metalcapCapEdge (enc < (lambda * 5.0)) errMesg)
executing: drc(metalcapCapEdge via4metalcapEdge (enc < (lambda * 3.0)) errMesg)
executing: drc(metalcapCapEdge via4Edge (sep < (lambda * 5.0)) errMesg)
executing: drc(metalcapCapEdge via3Edge (sep < (lambda * 5.0)) errMesg)
executing: saveDerived(geomAnd(metalcap via3) errMesg)
executing: drc(metalcapBottomEdge via4Edge (enc < (lambda * 5.0)) errMesg)
executing: drc(metalcapBottomEdge via3Edge (enc < (lambda * 5.0)) errMesg)
DRC started.....Thu Sep 22 16:03:54 2011
completed ....Thu Sep 22 16:03:55 2011
CPU TIME = 00:00:00 TOTAL TIME = 00:00:01
***** Summary of rule violations for cell "inverter layouttest" *****
Total errors found: 0
```

Help



1

mouse L: showClickInfo()


M: leHiMousePopUp()

R: setDRCForm()



3. LVS (Layout versus Schematic)

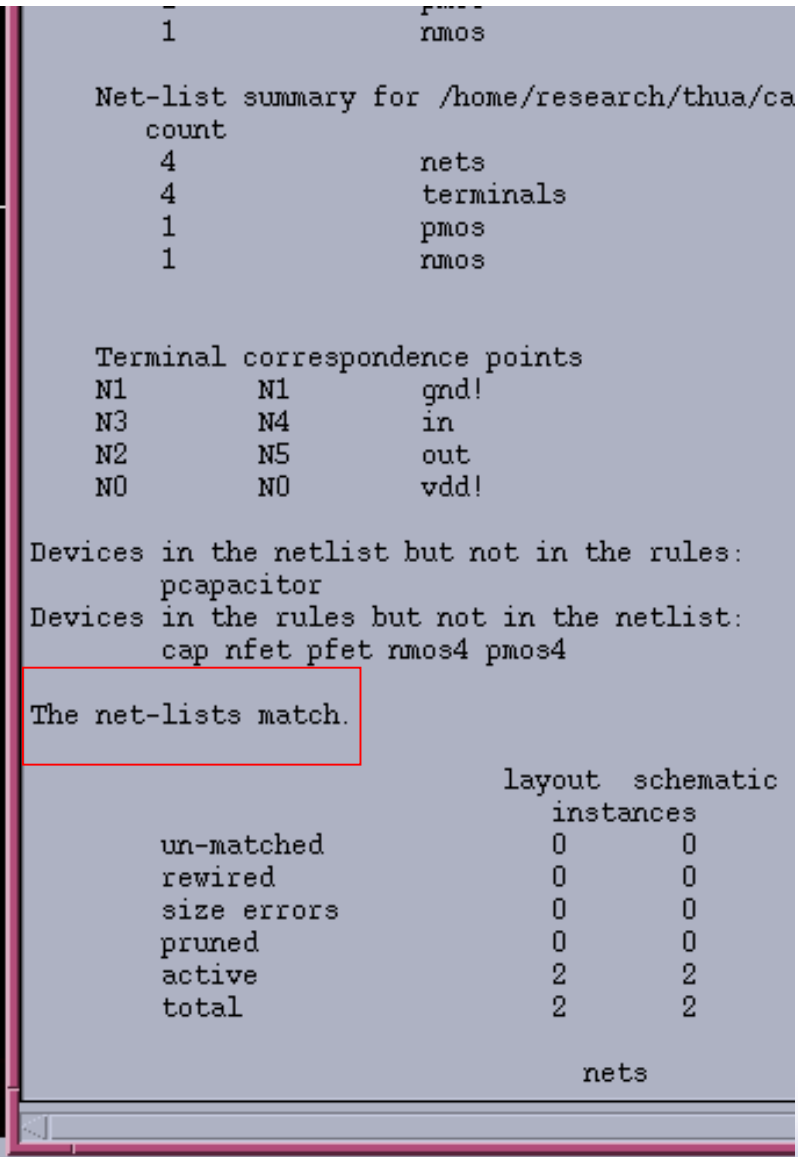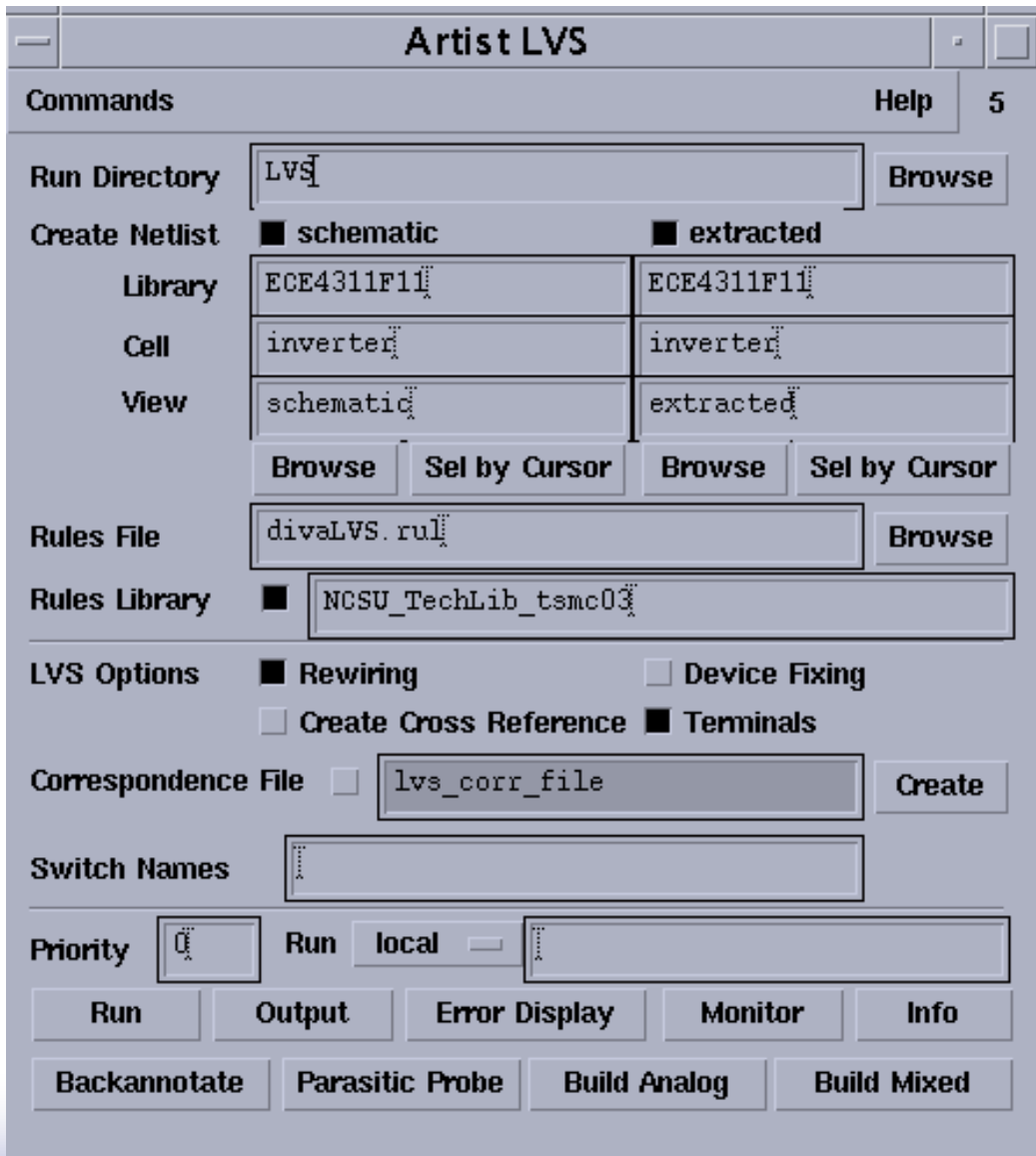

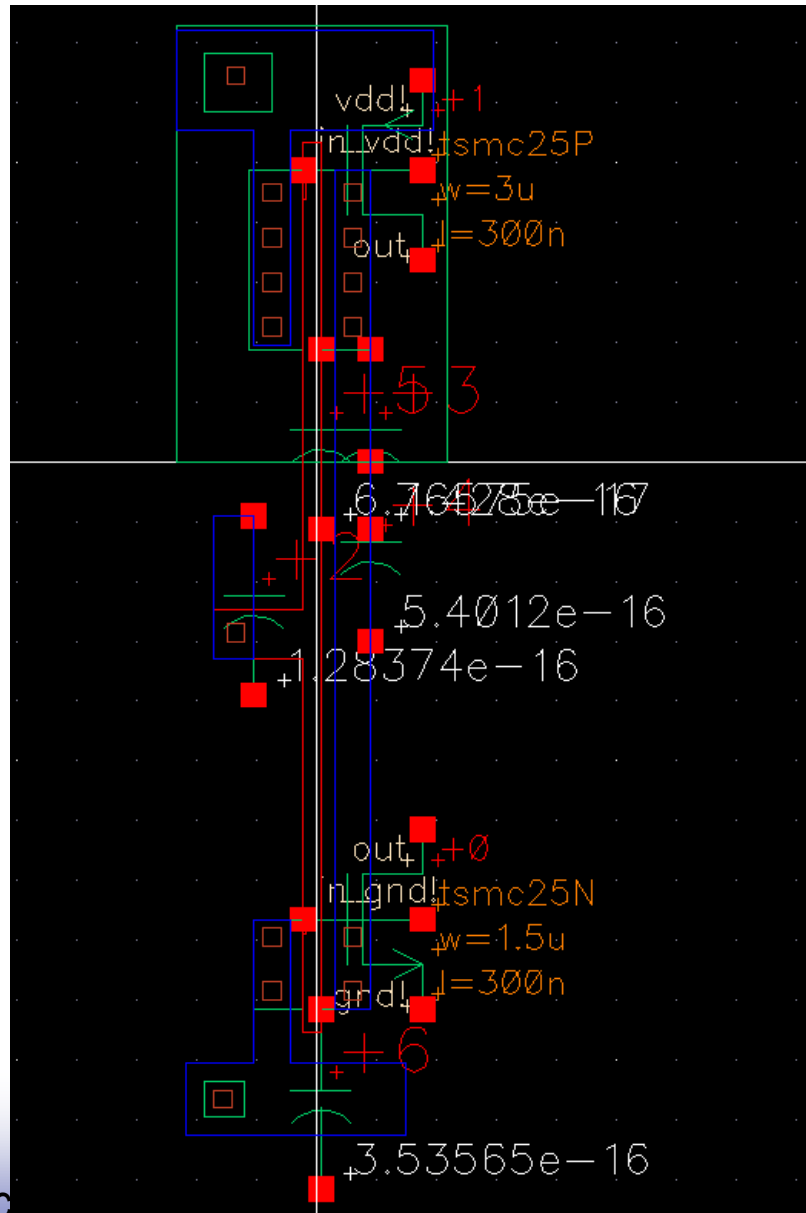4. Extract Layout parasitics and post-layout simulation





CMOS Inverter

  


Two Inverters

  Layout preference:
Share power and ground
Abut cells



Impact of Process Variations (DFM)


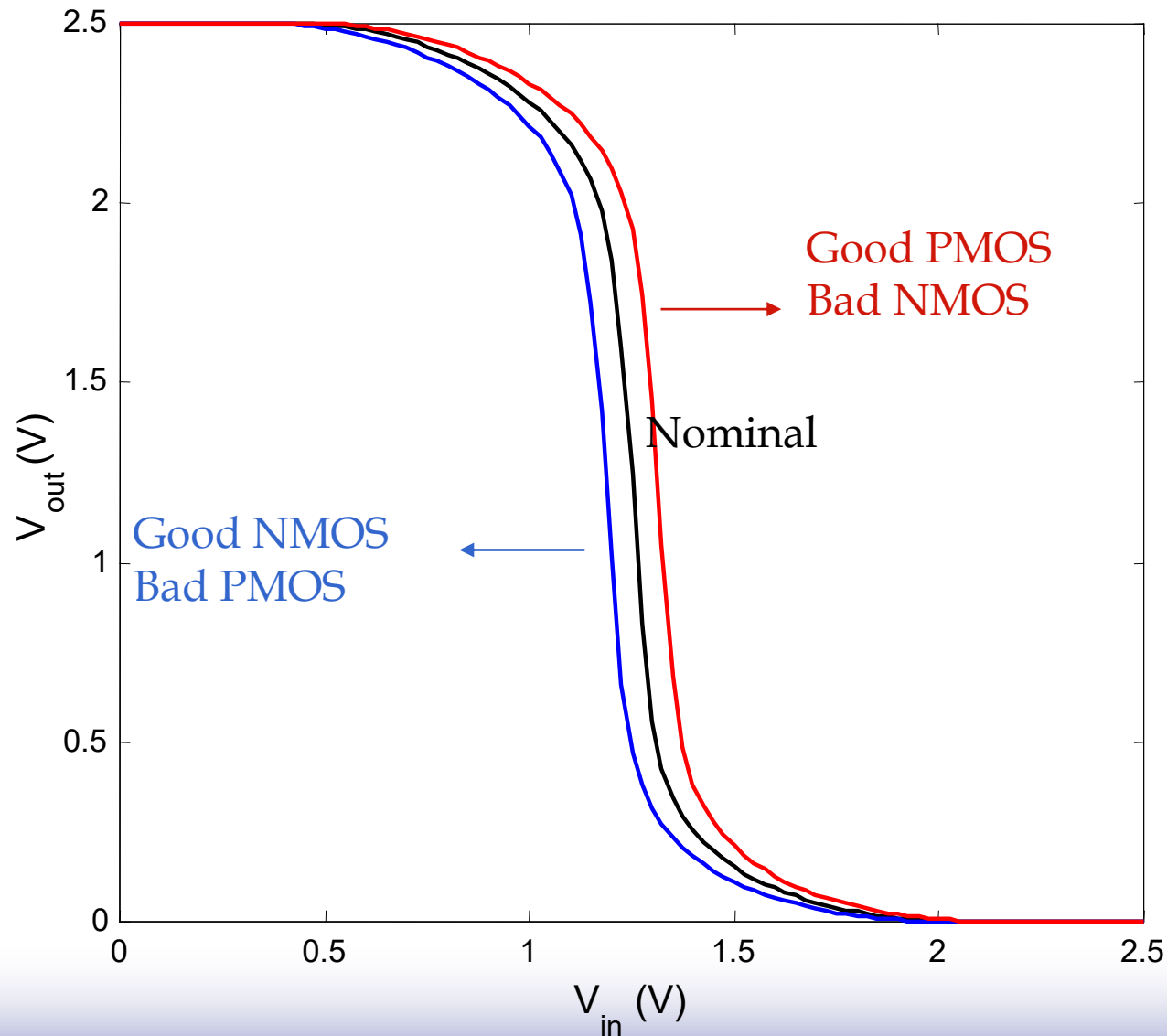




Inverter Sizing for delay

Inverter with Load

  W means the size is increased by a factor of W with respect to the minimum size



$$\begin{aligned} \text{Delay} &= kR_W(C_{int} + C_L) = kR_W C_{int} + kR_W C_L \\ &= \text{Delay (Internal)} + \text{Delay (Load)} \\ &= kR_W C_{int}(1 + C_L / C_{int}) \end{aligned}$$

Delay as function of size

$$\begin{aligned}\text{Delay} &= kR_W C_{int}(1 + C_L / C_{int}) \\ &= \text{Delay (Internal)} + \text{Delay (Load)}\end{aligned}$$

$$R_W = R_{unit} / W ; C_{int} = W C_{unit}$$

$$t_p = t_{p0} (1 + C_L / (W C_{unit}))$$

$$t_{p0} = 0.69 R_{unit} C_{unit}$$

- *Intrinsic delay is fixed and independent of size W*
- Making W large yields better performance gain, eliminating the impact of external load and reducing the delay to intrinsic only. But smaller gain at penalty of silicon area if W is too large!

Delay Formula

$$\text{Delay} \sim R_W (C_{int} + C_L)$$

$$t_p = kR_W C_{int} (1 + C_L / C_{int}) = t_{p0} (1 + f / \gamma)$$

$C_{int} = \gamma C_{gin}$ with $\gamma \approx 1$ for modern technology
(see page 199 in book or Slid 14 for an example)

C_{gin} : input gate capacitance

$C_L = f C_{gin}$ - effective fanout


This formula maps the intrinsic capacitor and load capacitor as functions of **a common capacitor**, which is the gate capacitance of the minimum-size inverter

Single inverter versus inverter chain

- ❑ Gate sizing for an isolated gate is not really meaningful. Realistic chips always have a long chain of gates.

- ❑ So, a more relevant and realistic problem is to determine the optimal sizing for a chain of gates.

Inverter Chain

 


If C_L is given:

- How many stages are needed to minimize the delay?
- How to size the inverters?

Apply to Inverter Chain (fixed N stages)

Unit size (minimum size) inverter

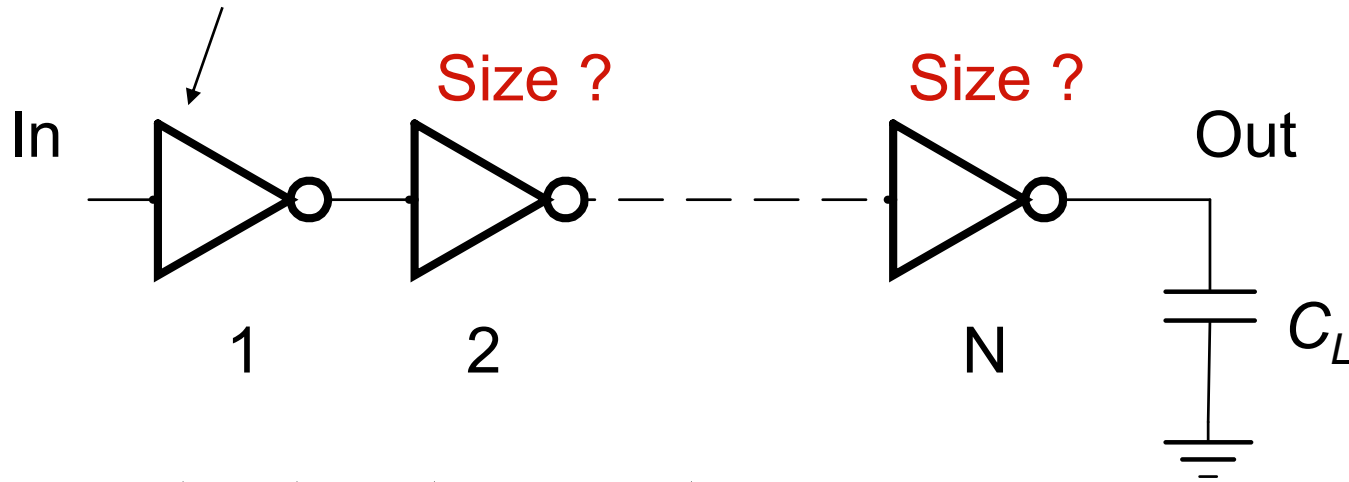

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{pj} \sim R_{unit} C_{unit} \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right)$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{i=1}^N \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right), \quad C_{gin,N+1} = C_L$$

Optimal Tapering for Given N

- Delay equation has $N - 1$ unknowns, $C_{gin,2} - C_{gin,N}$
- Minimize the delay, find $N - 1$ partial derivatives equated to 0
- Result: $C_{gin,j+1}/C_{gin,j} = C_{gin,j}/C_{gin,j-1}$
- Size of each stage is the geometric mean of two neighbors

$$C_{gin,j} = \sqrt{C_{gin,j-1} C_{gin,j+1}}$$

- *each stage has the same effective fanout*
- *each stage has the same delay*

Optimum Delay for fixed N stages

When each stage is sized by f and has same effective fanout f :

$$f^N = F = C_L / C_{gin,1} \longleftarrow \text{effective fanout of the overall circuit}$$


Effective fanout of each stage:

$$f = \sqrt[N]{F}$$

Minimum path delay

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{i=1}^N \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right) = N t_{p0} (1 + \sqrt[N]{F} / \gamma)$$

Example

 

C_L/C_1 has to be evenly distributed across $N = 3$ stages:

$$f = \sqrt[3]{8} = 2$$

Optimum Number of Stages

For a given load C_L and given input capacitance C_{in}
Find optimal sizing f

$$C_L = F \cdot C_{in} = f^N C_{in} \quad \text{with} \quad N = \frac{\ln F}{\ln f}$$

$$t_p = N t_{p0} \left(F^{1/N} / \gamma + 1 \right) = \frac{t_{p0} \ln F}{\gamma} \left(\frac{f}{\ln f} + \frac{\gamma}{\ln f} \right)$$

$$\frac{\partial t_p}{\partial f} = \frac{t_{p0} \ln F}{\gamma} \cdot \frac{\ln f - 1 - \gamma/f}{\ln^2 f} = 0$$

For $\gamma = 0$, $f = e$, $N = \ln F$


$$f = \exp(1 + \gamma/f)$$

Optimum Effective Fanout f

Optimum f for given process defined by γ

$$f = \exp(1 + \gamma/f)$$

$$f_{opt} = 3.6 \text{ for } \gamma=1$$

 

Impact of introducing buffers

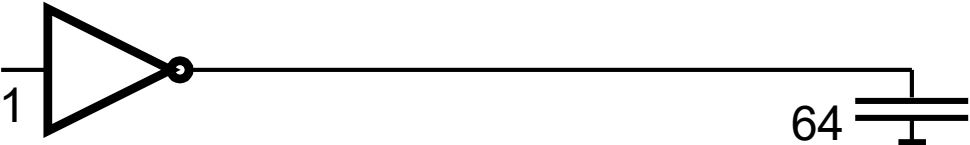
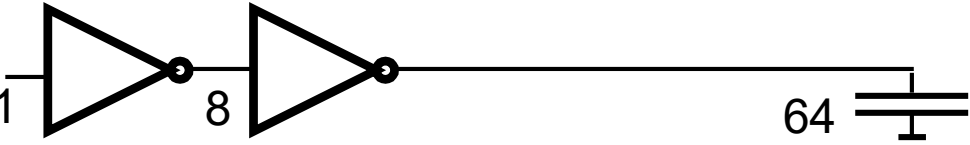
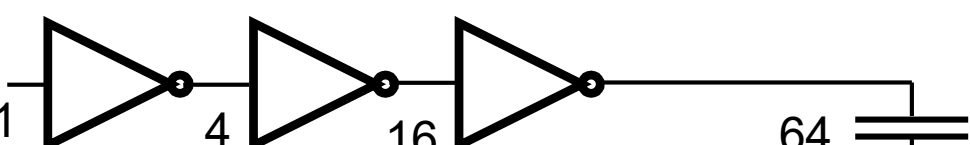

$$t_p = Nt_{p0} \left(1 + \sqrt[N]{F} / \gamma \right)$$

$$f_{opt} = 4$$




F	Unbuffered	Two Stage	Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1000	1001	65	24.8
10,000	10,001	202	33.1

Buffer Design

	N	f	t_p
	1	64	65
	2	8	18
	3	4	15
	4	2.8	15.3

Intel Itanium Microprocessor

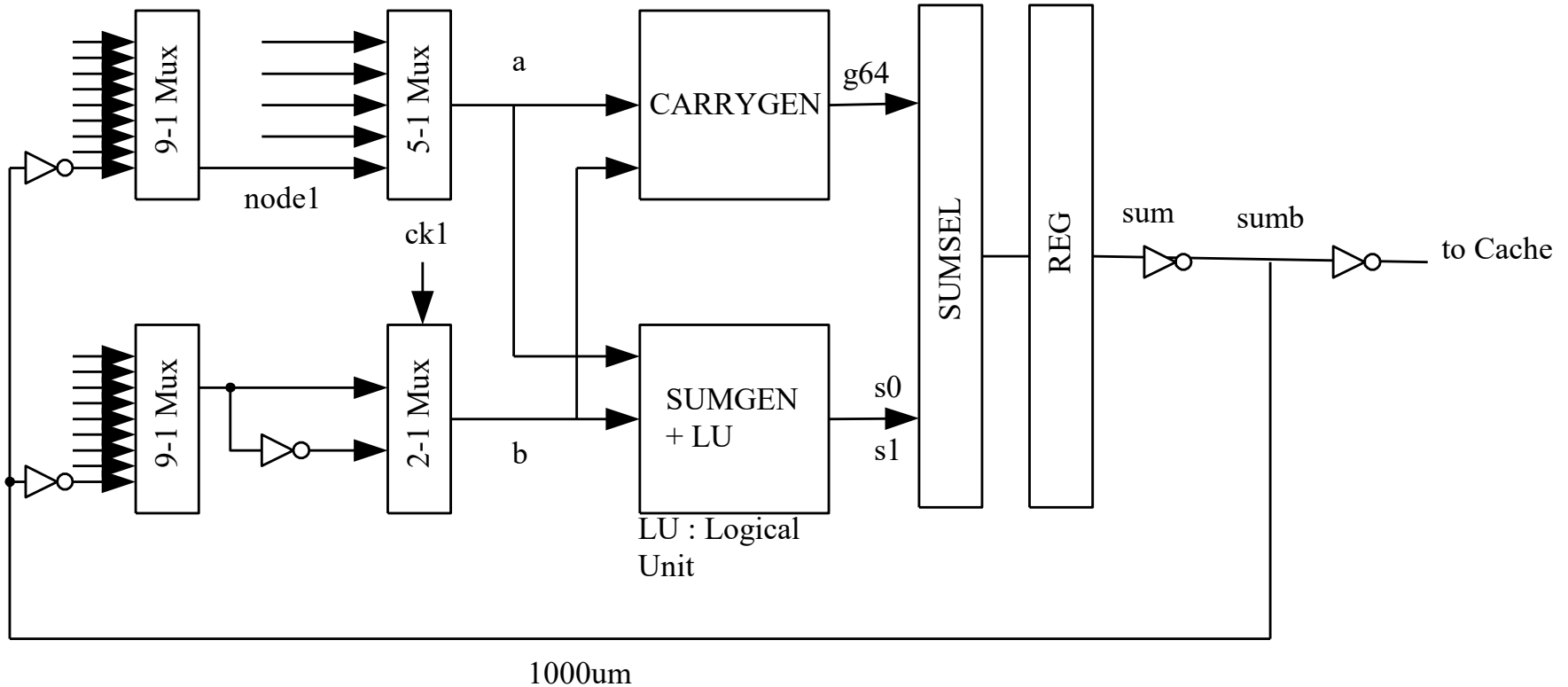

Itanium has 6 integer execution units like this