

HW #2


(i) 12 bit A/D converter 12 bits, $0 \leq V_{in} \leq 5.0V$

(a) Design circuit to allow V_{in} from $-10V$ to $+10V$ to be converted


(i) compress range to $\pm 2.5V \Rightarrow \div 4$

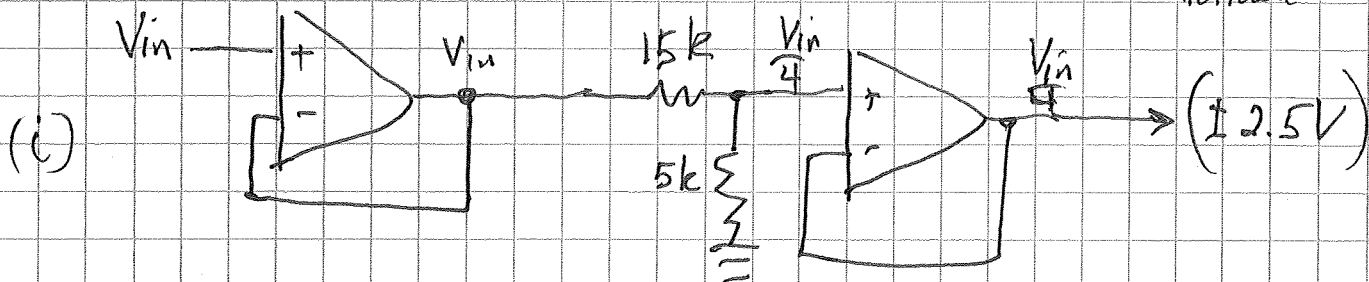(ii) shift to 0 to $+5V$

To draw little current start with a voltage follower with $\div 4$ divider after op-amp, then another follower!



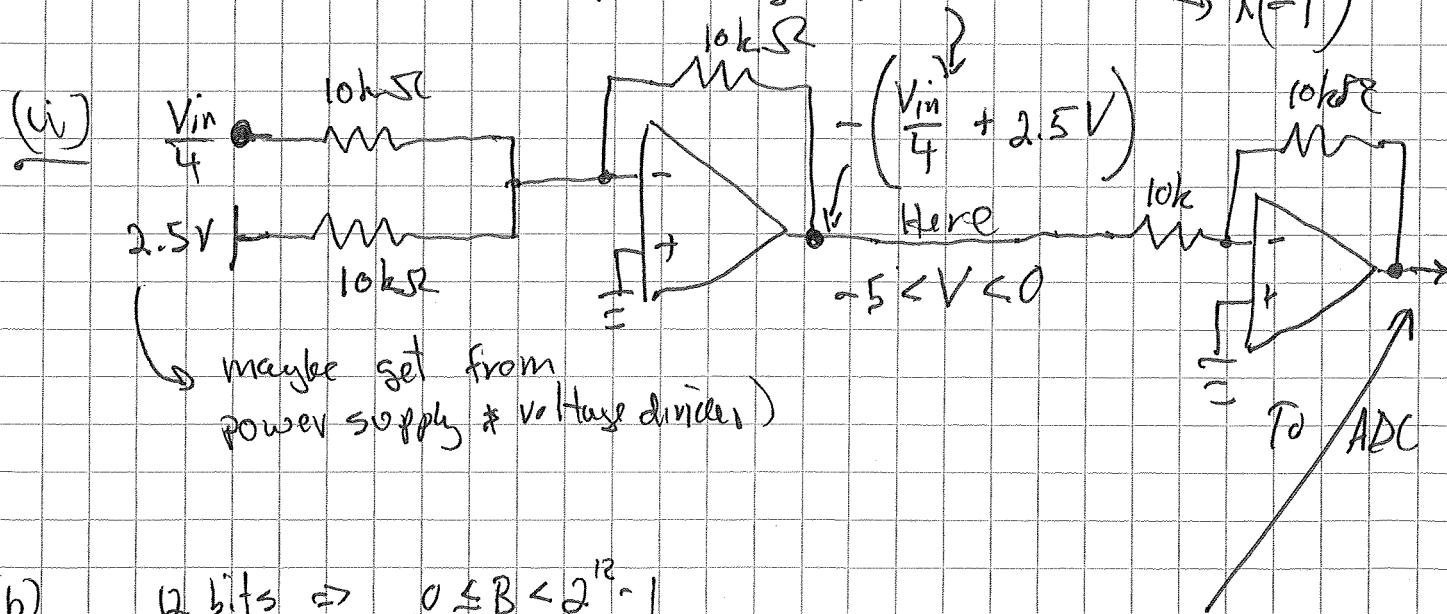Then shift with voltage adder and invert $\rightarrow \times (-1)$



(b) 12 bits $\Rightarrow 0 \leq B < 2^{12} - 1$

or 4096 values

so original input voltage $\pm 10V$ has a $20V$ range divided in 2^{12} steps

$0 \leq V_{ADC} \leq 5.0V$

$$\Delta V_{in} = \frac{20V}{2^{12}} = 4.88mV$$

so $\sim 5mV$ changes B output of ADC by 1 count (binary)

(2) Piezo scanner $\Delta X = \alpha \Delta V$

$$\alpha = 8.0 \frac{\text{nm}}{\text{V}}$$

$$\text{nm} = \text{nanometer} = 10^{-9} \text{ m}$$

12 bit DAC and $\pm 100 \text{ V}$ range \Rightarrow smallest

$$\Delta V = \frac{200 \text{ V}}{2^{12}} = 0.0488 \text{ V}$$

(a) And with total swing from -100 V to $+100 \text{ V}$

$$\frac{\text{biggest}}{\text{(total)}} \Delta X = \frac{8 \text{ nm}}{\text{V}} \cdot 200 \text{ V} = 1600 \text{ nm} = 1.6 \mu\text{m}$$

total travel

(b) Smallest step is $\Delta X_{\text{min}} = \frac{200 \text{ V}}{2^{12}} \cdot 8 \frac{\text{nm}}{\text{V}}$

$$= (48.8 \text{ mV}) \left(8.0 \frac{\text{nm}}{\text{V}} \right)$$

$$\Delta X_{\text{min}} = 0.39 \text{ nm} (= 3.9 \text{ \AA})$$

This is comparable to interatomic distances in a solid (a few $\times 0.1 \text{ nm}$)

(c) 16 bit DAC \Rightarrow smallest $\Delta V = \frac{200 \text{ V}}{2^{16}} = 3.05 \text{ mV}$

(4 more bits \Rightarrow 16x smaller steps)

$$\Delta X_{\text{min}} = \left(8.0 \frac{\text{nm}}{\text{V}} \right) \cdot (3.05 \text{ mV})$$

$$= 0.0244 \text{ nm} = 24.4 \text{ pm} \quad \downarrow 10^{-12}$$

($\approx \frac{1}{2}$ the Bohr radius of Hydrogen atom)