
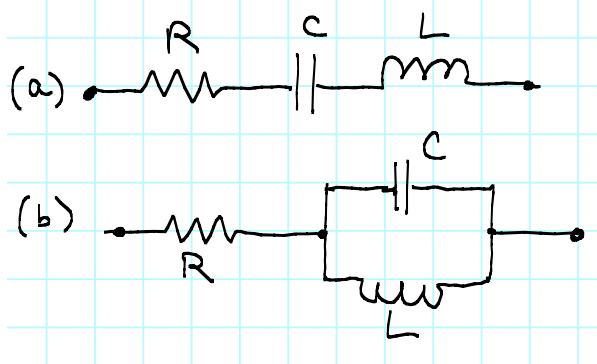


PHYS 5061 Homework 1
Due Wed. Feb. 13

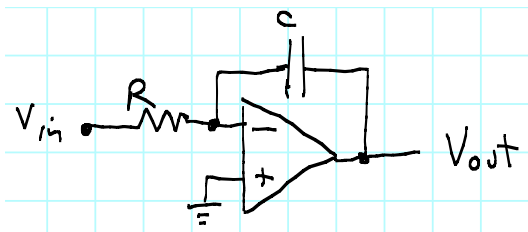- 1) The reciprocal of impedance is called admittance, often denoted by $Y=1/Z$. Instead of thinking $V = IZ$ as the generalization of Ohm's law $V=IR$, the admittance is handy in expressing the current as being proportional to voltage. $I = YV$. Consider the two RLC circuits at right. Assume they are each driven by a voltage $V(t) = V_0 e^{i\omega t}$. For (a) find the magnitude of the admittance $Y(\omega)$ as a function of frequency and. Sketch it qualitatively as a function of frequency. Where is the admittance a maximum and what is the maximum current that will flow? For circuit (b) find the magnitude of the impedance $Z(\omega)$. Sketch it. How does the current through this combination vary with frequency? At what frequency is it a minimum? What is the minimum current? What's the maximum current?



- 2) The op-amp circuit is connected to a time-dependent $V_{in}(t)$. Applying the golden rules for op-amps show that the output voltage is proportional to the time integral of $V_{in}(t)$: $V_{out}(t) = -(1/RC) \int V_{in}(t) dt$.



- 3) Apply the golden rules for op-amps to find an expression for $V_{out}(t)$ in terms of $V_{in}(t)$ for this circuit. Verify that for $V_{in}(t)$ restricted to the range of -5 V to $+5$ V, the output will be between 0 and -5 V.

