

## AC CIRCUITS

<b>Sinusoidal Waveforms:</b>	$v(t) = V_{\max} \cos(\omega t + \alpha)$ Volts	$i(t) = I_{\max} \cos(\omega t + \beta)$ Amps
<b>Phasors</b>	$V = V_{\text{rms}} \angle \alpha$ Volts	$I = I_{\text{rms}} \angle \beta$ Amps
<b>Angular Frequency, <math>\omega</math></b>	$\omega = 2\pi f$ Radians/Second $\omega = 377$ Rad/sec in North America $\omega = 314$ Rad/sec where 50 Hz is std.	In North America: $f = 60$ Hz Elsewhere, usually: $f = 50$ Hz
<b>Effective Value (RMS)</b>	$V_{\text{rms}} = V_{\max} / \sqrt{2}$ Volts	$I_{\text{rms}} = I_{\max} / \sqrt{2}$ Amps
<b>Ohm's Law</b>	for DC Circuits: $V = IR$	AC: $V = IZ$ ; Where V, I and Z are complex phasors.
<b>Complex Impedance, Z</b>	$Z = R + jX$ $Z =  Z  \angle \theta$	$jX_L = j\omega L$ (L in Henries) $-jX_C = 1/j\omega C$ (C in Farads)
<b>Complex Loads in Parallel</b>	$Z_{\text{eq}} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{Z_1 Z_2}{Z_1 + Z_2}$	

## AC POWER

<b>Instantaneous Power, p(t)</b>	$p(t) = v(t) i(t)$ Volt-Amperes	Product of sinusoidal signals
<b>Real Power (Effective Power)</b>	$P = V_{\text{rms}} I_{\text{rms}} \cos \theta$ Watts	$V_{\text{rms}}$ and $I_{\text{rms}}$ are the <u>magnitudes</u> of the voltage and current phasors
<b>Power Factor, pf</b>	pf = $\cos \theta$ (no units) Either expressed as Per Unit or as Percent.	$\theta = \text{Angle}(V) - \text{Angle}(I)$ $= \tan^{-1}(X/R)$ $= \tan^{-1}(Q/P)$ $= \text{Angle}(Z)$
<b>Power Angle, <math>\theta</math></b>	If $\theta$ is Positive: pf is lagging, I lags V, and Q is Inductive	If $\theta$ is Negative: pf is leading, I leads V, and Q is Capacitive
<b>Reactive Power, Q</b>	$Q = V_{\text{rms}} I_{\text{rms}} \sin \theta$ VARs	Volt-Amperes – Reactive (VAR)
<b>Apparent Power,  S </b>	$ S  =  V   I $ Volt-Amperes	Product of Voltage and Current magnitudes
<b>Complex Power, S</b>	$S = V I^*$ or $S = P + jQ$	Product of Voltage Phasor and the complex conjugate of the Current Phasor: $I^* = I_{\text{rms}} \angle -\theta_I$

## 3-PHASE AC CIRCUITS and POWER:

**Note:** Always assume a given Voltage is Line Voltage, unless otherwise specified.

<b>Phase Voltage, <math>V_{\text{Phase}}</math></b>	$V_{\text{Phase}} = V_{L-N}$ (Phase Voltage is often called the Line-to-Neutral Voltage)	In a WYE system. Phase Voltage is the voltage of a phase with respect to the neutral point of the WYE.
<b>Line Voltage, <math>V_{\text{Line}}</math></b>	$V_{\text{Line}} = V_{L-L}$ (Line Voltage is often called the Line-to-Line Voltage)	In a WYE or a DELTA system the Line Voltage is measured at one phase with respect to another phase.
<b>WYE Source or Load:</b>	$V_{\text{Line}} = \sqrt{3} V_{\text{Phase}} \angle +30^\circ$	$I_{\text{Line}} = I_{\text{Phase}}$
<b>DELTA Source or Load:</b>	$V_{\text{Line}} = V_{\text{Phase}}$	$I_{\text{Line}} = \sqrt{3} I_{\text{Phase}} \angle -30^\circ$
<b>3-Phase Power, <math>P_{3\phi}</math></b>	$P_{3\phi} = \sqrt{3}  V_{\text{Line}}   I_{\text{Line}}  \cos \theta$ Watts	$Q_{3\phi} = \sqrt{3}  V_{\text{Line}}   I_{\text{Line}}  \sin \theta$ VARs
<b>3-Phase Apparent Power, <math> S_{3\phi} </math></b>	$ S_{3\phi}  = \sqrt{3}  V_{\text{Line}}   I_{\text{Line}} $ Volt-Amperes	